

XII Physics
English Medium
Study material
Important derivations steps
2022-2023

UNIT-2

Prepared by

Mr. G.THIRUMOORTHI M.Sc,B.Ed,(Ph.D)

Sir C.V. Raman Coaching centre

Idappadi (Tk)

Salem (Dt) - 637101

(8610560810, 8883610465)

எழில் நோய்கள் " EVEREST "
எழி வாய்திட நோய்கள் " NEVER REST "

022

Unit - 2Current ElectricityCurrent (I)

$$I = \frac{Q}{t}$$

 $I \rightarrow$ Current. $Q \rightarrow$ charge. $t \rightarrow$ time.charge = Current \times time

(q ion)

(I)

(t)

Unit :charge \rightarrow coulomb \rightarrow Ctime \rightarrow second \rightarrow scurrent \rightarrow ampere \rightarrow AQuantity :

Scalar Quantity.

Current density (J)

$$J = \frac{I}{A}$$

Current density = $\frac{\text{Current}}{\text{cross sectional area}}$

$$J = \frac{A}{\text{m} \times \text{m}}$$

$$J = \frac{A}{\text{m}^2}$$

$$J = \text{Am}^{-2}$$

Quantity:

Vector Quantity.

Current scalar $= \frac{Q}{t} = A$

Current density vector $\frac{I}{A} = \text{Am}^{-2}$

Current

$$I = \frac{Q}{t}$$

$$I = \frac{C}{S} = \text{Cs}^{-1}$$

$$\text{Ampere (or) } \text{Cs}^{-1}$$

Example 2.1

charge = 120 C

Copper wire.

time = 1 minute.

Current

$$Q = 120 \text{ C.}$$

$$I = \frac{Q}{t}$$

$$I = \frac{120}{60}$$

$$I = 2 \text{ A}$$

$$t = 1 \text{ minute.}$$

$$= 1 \times 60 \text{ seconds.}$$

Creative Question.

$$\text{charge} = 120 \text{ C}$$

Copper wire

$$\text{time} = 1 \text{ second.}$$

Current

$$I = \frac{Q}{t}$$

$$I = \frac{120}{1}$$

$$I = 120 \text{ A}$$

05-07-2022

ohm's law.
(ஒம்ஸ் கூறி)

$$V = IR$$

$$I \propto V$$

R → Resistance

I → current.

V → potential difference.

(volt)

Voltage.

I → current → Ampere → A

V → Potential difference → volt → V

R → Resistance → ohm → Ω


R ↑ I ↓

I ↑ V ↑

I ↓ V ↓

$A \rightarrow$ current \rightarrow Ammeter.

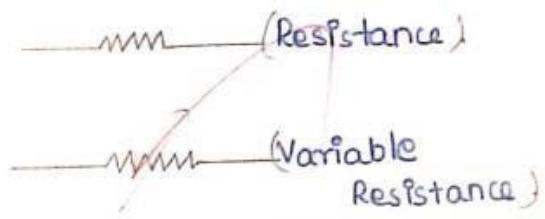
$V \rightarrow$ potential difference \rightarrow voltmeter.



pg no: 28
Ex. 2.5

Example 2.5

Soln.

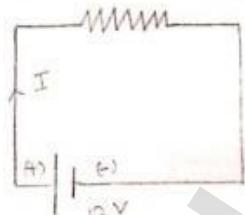

$$R = 24 \Omega$$

$$V = 12 V$$

$$I = ?$$

Applying Ohm's law

$$V = IR$$

$$I = \frac{R}{V}$$

$$I = \frac{24}{12} = \frac{1}{2}$$

$$I = 0.5 A$$

Ex. 2.4

Soln.

number of electrons, $n = ?$

$$t = 1 \text{ sec}$$

$$I = 32 A$$

Current

$$I = \frac{Q}{t} = \frac{q}{t}$$

Quantisation of charge

$$q = ne$$

$$I = \frac{q}{t}$$

$$I = \frac{ne}{t}$$

$$It = ne$$

$$n = \frac{It}{e}$$


$$e = 1.6 \times 10^{-19} C$$


$$n = \frac{32 \times 1}{1.6 \times 10^{-19}}$$

$$n = \frac{32}{1.6} \times 10^{19}$$

$$n = 20 \times 10^{19}$$

$$n = 2 \times 10^{20} \text{ electrons}$$

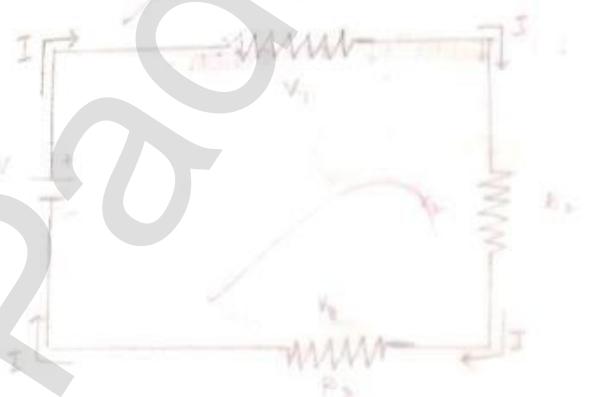Resistor series connection

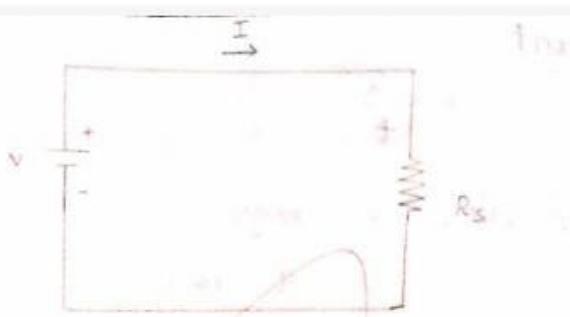

Resistor series connection
 $V = V_1 + V_2 + V_3$

Applying ohm's law

$$V = IR$$

$$V_1 = IR_1 \quad \text{---} \textcircled{1}$$

$$V_2 = IR_2 \quad \text{---} \textcircled{2} \quad I \rightarrow \text{constant}$$

$$V_3 = IR_3 \quad \text{---} \textcircled{3}$$

$$V = IR_1 + IR_2 + IR_3$$


$$V = IR_s$$


$$IR_s = IR_1 + IR_2 + IR_3$$

$$IR_s = I(R_1 + R_2 + R_3)$$

$$R_s = R_1 + R_2 + R_3$$

Resistor parallel connection.

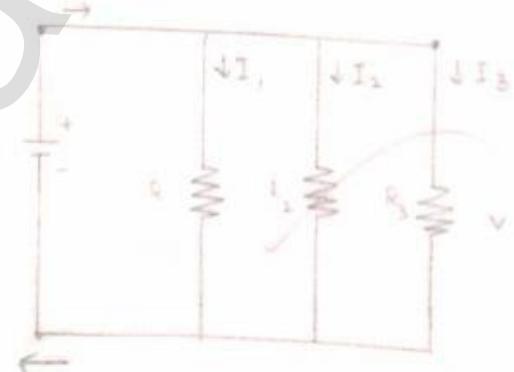

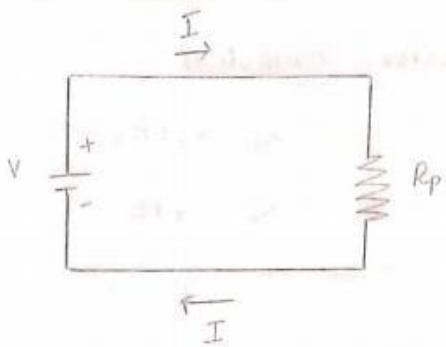

Resistor parallel connection.

$$I = I_1 + I_2 + I_3$$

Applying ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$

$V \rightarrow$ constant

$$I_1 = \frac{V}{R_1} \quad \text{---(1)}$$

$$I = I_1 + I_2 + I_3$$

$$I_2 = \frac{V}{R_2} \quad \text{---(2)}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I_3 = \frac{V}{R_3} \quad \text{---(3)}$$


$$I = \frac{V}{R_p}$$

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$V\left(\frac{1}{R_p}\right) = V\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Example 2.8

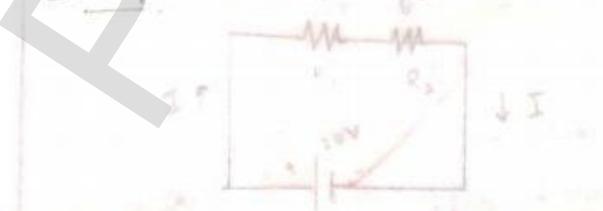

Series connection

$$R_s = R_1 + R_2$$

$$R_s = 4 + 6$$

$$R_s = 10 \Omega$$

current = ?

Applying Ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = R_s$$

$$I = \frac{V}{R_s}$$

$$I = \frac{24}{10}$$

$$I = 2.4 A$$

$$R_1 = 4 \Omega$$

$$I = 2.4 A$$

$$V_1 = IR_1$$

$$V_1 = 2.4 \times 4$$

$$V_1 = 9.6 V$$

$$R_2 = 6 \Omega$$

$$V_2 = IR_2$$

$$V_2 = 6 \times 2.4$$

$$V_2 = 14.4 V$$

(Resistance increase
Potential difference increase)

Creative Question

9Ω, 9Ω, 9Ω series and parallel.

Series :

$$R_s = R_1 + R_2 + R_3$$

$$R_s = 9 + 9 + 9$$

$$R_s = 27 \Omega$$

Parallel :

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{R_p} = \frac{3}{9}$$

$$\frac{1}{R_p} = \frac{1}{3}$$

$$R_p = 3 \Omega$$

2Ω and 4Ω series and parallel.

Series :

$$R_s = R_1 + R_2$$

$$R_s = 2 + 4$$

$$R_s = 6 \Omega$$

Parallel :

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{4}$$

$$\frac{1}{R_p} = \frac{2+1}{4} = \frac{3}{4}$$

$$R_p = \frac{4}{3} \Omega$$

Example 2.11

pg no : 93

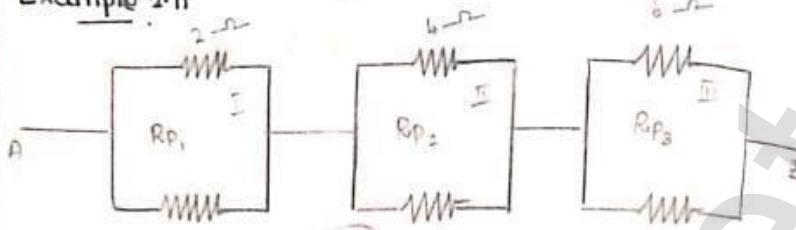

Parallel

$$\text{I. } \frac{1}{R_{p1}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{p1}} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2}$$

$$\frac{1}{R_{p1}} = 1$$

$$R_{p1} = 1 \Omega$$

$$\text{II. } \frac{1}{R_{p2}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{p2}} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4}$$

$$\frac{1}{R_{p2}} = \frac{1}{2}$$

$$R_{p2} = 2 \Omega$$

$$\text{III. } \frac{1}{R_{p3}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{p3}} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6}$$

$$\frac{1}{R_{p3}} = \frac{1}{3}$$

$$R_{p3} = 3 \Omega$$




series

$$R_s = R_{p1} + R_{p2} + R_{p3}$$


$$R_s = (1+2+3) \Omega$$

$$\boxed{R_s = 6 \Omega}$$

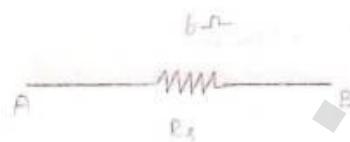

Example 2.9

pg no : 92

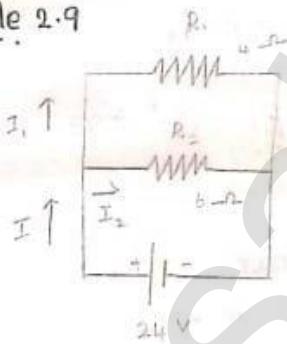

Resistance parallel connection.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6}$$

$$\frac{1}{R_p} = \frac{3+2}{12} = \frac{5}{12}$$

$$\boxed{R_p = \frac{12}{5} \Omega}$$

Applying ohm's law.

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_1 = \frac{V}{R_1}$$

$$I_1 = \frac{24}{4} = 6 \text{ A}$$

$$I_2 = \frac{V}{R_2}$$

$$I_2 = \frac{24}{6} = 4 \text{ A}$$

Total current,

$$I = I_1 + I_2$$

$$I = 6 + 4$$

$$\boxed{I = 10 \text{ A}}$$

Colour coding for resistors

Resistor

- (3) colour
- (1) tolerance

1. Orange, Orange, Orange, Gold tolerance

$$= 33000 \pm 5\%$$

$$= 33 \times 10^3 \pm 5\%$$

$$= 33 \times 10^3 \pm 5\%$$

$$\boxed{= 33 \text{ k}\Omega \pm 5\%}$$

2. Green, blue, orange, Gold tolerance.

$$= 56000 \pm 5\%$$

$$\boxed{= 56 \text{ k}\Omega \pm 5\%}$$

3. Blue, Gray, Red, colourless.

$$= 6800 \pm 20\%$$

$$= 68 \times 10^2 \Omega \pm 20\%$$

4. Violet, yellow, Red.

$$= 7400$$


$$= 74 \times 10^2 \Omega \pm 20\%$$

5. Blue, red, Green

$$= 62 \times 10^5 \Omega \pm 20\%$$

5M.
pg no. 85.

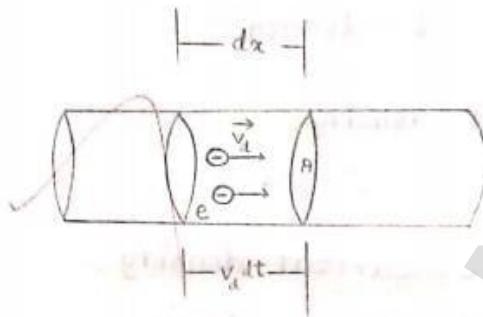Microscopic model of current and Ohm's law :



Current

$$I = \frac{dQ}{dt}$$

$$dQ = nAe v_d dt$$

$A \rightarrow$ cross sectional area.

$e \rightarrow$ electron.

$v_d \rightarrow$ drift velocity.

$$I = \frac{nAe v_d dt}{dt}$$

$$I = nAe v_d$$

Current density :

$$J = \frac{I}{A}$$

$$J = \frac{nAe v_d}{A}$$

$$J = ne v_d \quad \text{--- (2)}$$

Drift velocity :

$$v_d = -\frac{e\tau}{m} E$$

$\tau \Rightarrow$ Average time.

$E \Rightarrow$ Electric field.

$m \Rightarrow$ mass

$e \Rightarrow$ electron

$$J = ne \left(-\frac{e\tau}{m} E \right)$$

$$J = -\frac{ne^2\tau}{m} E$$

$$\boxed{J = -\sigma E} \quad -③$$

vector form :

$$\vec{J} = \sigma \vec{E}$$

conductivity :

$$\boxed{\sigma = \frac{ne^2\tau}{m}}$$

$$\rho = \frac{1}{\sigma}$$

Resistivity :

$$\rho = \frac{1}{ne^2\tau} \frac{1}{m}$$

$$\boxed{\rho = \frac{m}{ne^2\tau}}$$