

**SIR C.V RAMAN COACHING CENTRE ,IDAPPADI,SALEM-637101**

SUB: PHYSICS STD : XII Time : 1.00 hrs

Date : 11.06.2023

UNIT : 2 Current Electricity Total mark : 35m

.....  
**Dr.G.THIRUMOORTHY ,M.Sc,B.Ed,Ph.D ,(physics)**

Assistant professor ,Govt Arts college salem -7 ,(8610560810),,  
(8883610465)

.....  
Section – A ( 5 x 1 = 5m )

I.Choose the best correct answer

1.A 110 W,220 V bulb draws a current

a) 2A b) 440 A c) 0.5 A d) 5.5A

2. 5 A of current flowing through resistor for 2 minute produce 3000 j of heat the value of the resistance is .....

a) 1 ohm b) 2 ohm c) 4 ohm d) 5 ohm

3.Choose the odd one out

a) Current density b) current c) drift velocity d) Electric field

4. The one of the resistors in a parallel circuit is removed the total resistance will be .....

a) Doubled b) decreases c) increases d)constant

5. The unit of conductivity is .....

a) mho b) ohm c) ohm-m d) mho – m<sup>-1</sup>

Section – B ( 5 X 3 = 15 m)

II. Answer any FIVE questions

6. The resistance of a wire is 20 ohm what will be new resistance if it is stretched uniformly Eight times its original length?
7. Relation between current and drift velocity
8. The resistance of a Nichrome wire at  $20^{\circ}\text{C}$  is 10 ohm if its temperature coefficient of resistivity of nichrome is  $0.004/^{\circ}\text{C}$ . find the resistance of the wire at boiling point of water comment on the result
9. (i) Define Electric cell (ii) find 1 Kwh
10. Derive the expression for power  $P = VI$  in electrical circuits
11. Explain potentiometer with neat circuit
12. Prove that  $H = I^2Rt$

Section – C ( 3 x 5 = 15 m)

III. Answer any THREE questions

13. Obtain the macroscopic form of ohm's law from its microscopic form and discuss its limitation in graph analysis .
14. Determine the number of electrons flowing per second through a conductor when a current of 32 A flow's through it
15. Derive the expression for resultant cell when cell are connected in (i) Series and (ii) parallel connections with neat diagram
16. (i) How will you represent a resistor of 3700 ohm and 10 % by color code  
(ii) Find the resistance series and parallel connection in 2 ohm, 4 ohm ,6 ohm ?
- 17 (i) Write the formula and unit a) Acceleration b) mobility c) drift velocity

(ii) Find the resistance value in 100 W – 220 V

Dr.G.THIRUMOORTHY