

SRIMAAN COACHING CENTRE-TRICHY-TN-MAWS- MUNICIPAL

ADMINISTRATION & WATER SUPPLY DEPARTMENT- EEE-(ELECTRICAL)

STUDY MATERIAL -TO CONTACT:8072230063.

2024-25

SRIMAAN

SRIMAAN

TN MAWS

MUNICIPAL ADMINISTRATION & WATER SUPPLY DEPARTMENT-(MAWS)

EEE-Assistant Engineer (Electrical)

TN-MAWS MATERIALS

**CIVIL/ MECHANICAL / EEE/ TOWN PLANNING/
ARCHITECTURE / PUBLIC HEALTH & SANITATION
AVAILABLE.**

**UG-TRB-(SGT)-STUDY MATERIAL (TAMIL &
ENGLISH MEDIUM) AVAILABLE.**

**PG-TRB STUDY MATERIALS:-TAMIL/ENGLISH/ MATHEMATICS/ PHYSICS
CHEMISTRY/COMMERCE (T/M & E/M)/BOTANY (T/M & E/M)/ ZOOLOGY
HISTORY (T/E)/ECONOMICS (T/E)/ GEOGRAPHY /BIO-CHEMISTRY**

PGTRB-COMPUTER INSTRUCTOR GRADE-I -TO CONTACT -8072230063.

Kindly send me your key answers to our email id - padkocai@rediffmail.com

SRIMAAN COACHING CENTRE-TRICHY-TNMAWS- MUNICIPAL

2024-25

ADMINISTRATION & WATER SUPPLY DEPARTMENT- EEE-(ELECTRICAL)

SRIMAAN

STUDY MATERIAL -TO CONTACT:8072230063.

TRB-POLYTECHNIC LECTURER MATERIALS:

**MATHEMATICS / ENGLISH / PHYSICS / CHEMISTRY / COMPUTER SCIENCE / IT /
EEE / ECE / EIE / ICE / MECHANICAL / CIVIL / MOP AVAILABLE.**

UG-TRB & SGT: ALL SUBJECT STUDY MATERIALS AVAILABLE.

SCERT/DIET/GTTI STUDY MATERIAL AVAILABLE.

DEO & BEO (T/M & E/M) STUDY MATERIALS AVAILABLE.

TRB-ASST.PROFESSOR STUDY MATERIAL AVAILABLE.

**PG-TRB: COMPUTER INSTRUCTOR GRADE-1 -FULL
STUDY MATERIAL WITH QUESTION BANK AVAILABLE**

**TNPSC-ASSISTANT DIRECTOR OF CO-OPERATIVE AUDIT STUDY
MATERIAL AVAILABLE.**

TNEB-(ASSESSOR/AE/JA) MATERIALS WITH QUESTION BANK AVAILABLE

**UG-TRB / PG-TRB / TRB-POLYTECHNIC / DEO & BEO
MATERIALS ARE SENDING THROUGH COURIER.**

TO CONTACT

8072230063

**PG-TRB STUDY MATERIALS:-TAMIL/ENGLISH/ MATHEMATICS/ PHYSICS
CHEMISTRY/ COMMERCE (T/M & E/M)/ BOTANY (T/M & E/M)/ ZOOLOGY
HISTORY (T/E)/ ECONOMICS (T/E)/ GEOGRAPHY / BIO-CHEMISTRY**

PGTRB-COMPUTER INSTRUCTOR GRADE-1 -TO CONTACT -8072230063.

Kindly send me your key answers to our email id - padkocai@gmail.com



SRIMAAN COACHING CENTRE-TRICHY.

TO CONTACT:8072230063.



**MUNICIPAL ADMINISTRATION & WATER SUPPLY DEPARTMENT
(TN-MAWS)**

**Paper-I-ELECTRICAL ENGINEERING
(Degree Standard)**


UNIT - I: ELECTRICAL CIRCUITS

CODE:103

Introduction: We now know that an ideal current source provides a specified amount of current completely independent of the voltage across it and as such will produce whatever voltage is necessary to maintain the required current. This then makes it completely independent of the circuit to which it is connected to resulting in it being called an ideal independent current source.

Generally, an ideal current dependent source, either voltage or current controlled is designated by a diamond-shaped symbol where an arrow indicates the direction of the current.

Dependent Current Source Symbols:

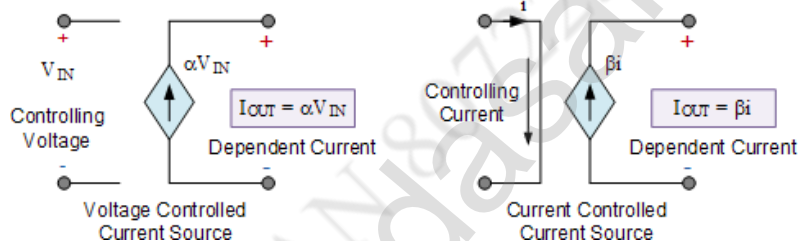

An ideal dependent voltage-controlled current source, VCCS, maintains an output current, I_{OUT} that is proportional to the controlling input voltage, V_{IN} . In other words, the output current “depends” on the value of input voltage making it a dependent current source.

Then the VCCS output current is defined by the following equation: $I_{OUT} = \alpha V_{IN}$. This multiplying constant α (alpha) has the SI units of mhos, \mathcal{U} (an inverted Ohms sign) because $\alpha = I_{OUT}/V_{IN}$, and its units will therefore be amperes/volt.

An ideal dependent current-controlled current source, CCCS, maintains an output current that is proportional to a controlling input current. Then the output current “depends” on the value of the input current, again making it a dependent current source.

As a controlling current, I_{IN} determines the magnitude of the output current, I_{OUT} times the magnification constant β (beta), the output current for a CCCS element is determined by the following equation: $I_{OUT} = \beta I_{IN}$. Note that the multiplying constant β is a dimensionless scaling factor as $\beta = I_{OUT}/I_{IN}$, so therefore its units would be amperes/amperes.

KVL

Kirchhoff's Voltage Law

Kirchhoff's Voltage Law (KVL) is Kirchhoff's second law that deals with the conservation of energy around a closed circuit path.

Gustav Kirchhoff's Voltage Law is the second of his fundamental laws we can use for circuit analysis. His voltage law states that for a closed loop series path **the algebraic sum of all the voltages around any closed loop in a circuit is equal to zero**. This is because a circuit loop is a closed conducting path so no energy is lost.

In other words the algebraic sum of ALL the potential differences around the loop must be equal to zero as: $\sum V = 0$. Note here that the term "algebraic sum" means to take into account the polarities and signs of the sources and voltage drops around the loop.


This idea by Kirchhoff is commonly known as the **Conservation of Energy**, as moving around a closed loop, or circuit, you will end up back to where you started in the circuit and therefore back to the same initial potential with no loss of voltage around the loop. Hence any voltage drops around the loop must be equal to any voltage sources met along the way.

So when applying Kirchhoff's voltage law to a specific circuit element, it is important that we pay special attention to the algebraic signs, (+ and -) of the voltage drops across elements and the emf's of sources otherwise our calculations may be wrong.

But before we look more closely at Kirchhoff's voltage law (KVL) let's first understand the voltage drop across a single element such as a resistor.

Circuit elements

A Single Circuit Element

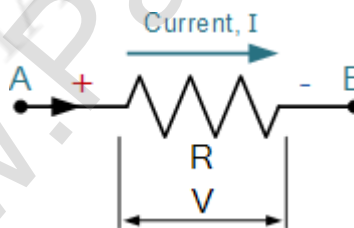

For this simple example we will assume that the current, I is in the same direction as the flow of positive charge, that is conventional current flow.

Here the flow of current through the resistor is from point A to point B, that is from positive terminal to a negative terminal. Thus as we are travelling in the same direction as current flow, there will be a *fall* in potential across the resistive element giving rise to a $-IR$ voltage drop across it.


If the flow of current was in the opposite direction from point B to point A, then there would be a *rise* in potential across the resistive element as we are moving from a -potential to a + potential giving us a $+I \cdot R$ voltage drop.

Thus to apply Kirchhoff's voltage law correctly to a circuit, we must first understand the direction of the polarity and as we can see, the sign of the voltage drop across the resistive element will depend on the direction of the current flowing through it. As a general rule, you will lose potential in the same direction of current across an element and gain potential as you move in the direction of an emf source.

The direction of current flow around a closed circuit can be assumed to be either clockwise or anticlockwise and either one can be chosen. If the direction chosen is different from the actual direction of current flow, the result will still be correct and valid but will result in the algebraic answer having a minus sign.

To understand this idea a little more, let's look at a single circuit loop to see if Kirchhoff's Voltage Law holds true.

A Single Circuit Loop

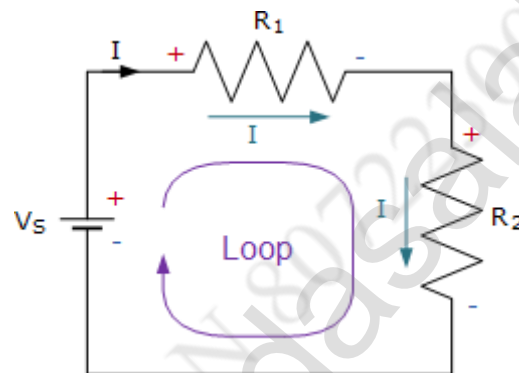

Kirchhoff's voltage law states that the algebraic sum of the potential differences in any loop must be equal to zero as: $\sum V = 0$. Since the two resistors, R_1 and R_2 are wired together in a series connection, they are both part of the same loop so the same current must flow through each resistor.

Thus the voltage drop across resistor, $R_1 = I \cdot R_1$ and the voltage drop across resistor, $R_2 = I \cdot R_2$ giving by KVL:

$$V_S + (-IR_1) + (-IR_2) = 0$$

$$\therefore V_S = IR_1 + IR_2$$

$$V_S = I(R_1 + R_2)$$

$$V_S = IR_T$$

$$\text{Where: } R_T = R_1 + R_2$$

We can see that applying Kirchhoff's Voltage Law to this single closed loop produces the formula for the equivalent or total resistance in the series circuit and we can expand on this to find the values of the voltage drops around the loop.

$$R_T = R_1 + R_2$$

$$I = \frac{V_S}{R_T} = \frac{V_S}{R_1 + R_2}$$

$$V_{R1} = IR_1 = V_S \left(\frac{R_1}{R_1 + R_2} \right)$$

$$V_{R2} = IR_2 = V_S \left(\frac{R_2}{R_1 + R_2} \right)$$

Kirchhoff's Voltage Law

Three resistor of values: 10 ohms, 20 ohms and 30 ohms, respectively are connected in series across a 12 volt battery supply. Calculate: a) the total resistance, b) the circuit current, c) the current through each resistor, d) the voltage drop across each resistor, e) verify that Kirchhoff's voltage law, KVL holds true.

a) Total Resistance(R_T)

$$R_T = R_1 + R_2 + R_3 = 10\Omega + 20\Omega + 30\Omega = 60\Omega$$

Then the total circuit resistance R_T is equal to 60 Ω

b) Circuit Current(I)

$$I = \frac{V_S}{R_T} = \frac{12}{60} = 0.2A$$

Thus the total circuit current I is equal to 0.2 amperes or 200mA

c) Current Through Each Resistor

The resistors are wired together in series, they are all part of the same loop and therefore each experience the same amount of current. Thus:

$$I_{R1} = I_{R2} = I_{R3} = I_{SERIES} = 0.2 \text{ amperes}$$

d) Voltage Drop Across Each Resistor

$$V_{R1} = I \times R_1 = 0.2 \times 10 = 2 \text{ volts}$$

$$V_{R2} = I \times R_2 = 0.2 \times 20 = 4 \text{ volts}$$

$$V_{R_3} = I \times R_3 = 0.2 \times 30 = 6 \text{ volts}$$

e) Verify Kirchhoff's Voltage Law

$$V_S + (-IR_1) + (-IR_2) + (-IR_3) = 0$$

$$12 + (-0.2 \times 10) + (-0.2 \times 20) + (-0.2 \times 30) = 0$$


$$12 + (-2) + (-4) + (-6) = 0$$

$$\therefore 12 - 2 - 4 - 6 = 0$$

Thus Kirchhoff's voltage law holds true as the individual voltage drops around the closed loop add up to the total.

KCL

Kirchhoff's Circuit Loop

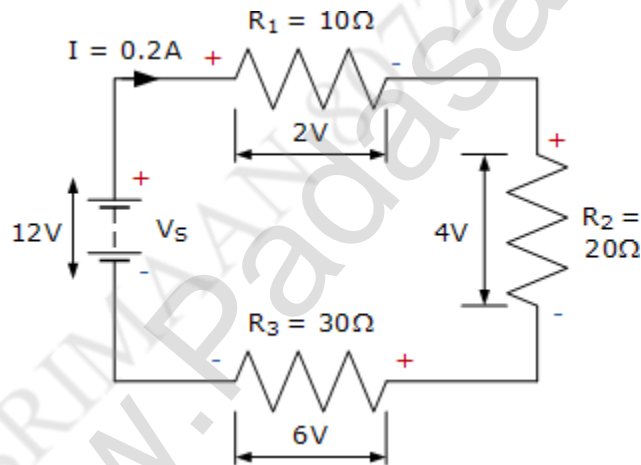


We have seen here that Kirchhoff's voltage law, KVL is Kirchhoff's second law and states that the algebraic sum of all the voltage drops, as you go around a closed circuit from some fixed point and return back to the same point, and taking polarity into account, is always zero. That is $\Sigma V = 0$

The theory behind Kirchhoff's second law is also known as the law of conservation of voltage, and this is particularly useful for us when dealing with series circuits, as series circuits also act as voltage dividers and the voltage divider circuit is an important application of many series circuits.

Kirchhoff's Current Law

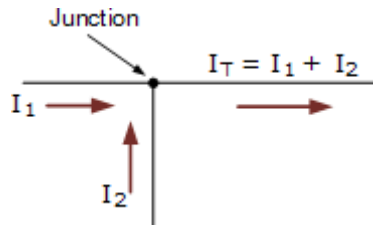Kirchhoff's Current Law (KCL) is Kirchhoff's first law that deals with the conservation of charge entering and leaving a junction.




To determine the amount or magnitude of the electrical current flowing around an electrical or electronic circuit, we need to use certain laws or rules that allows us to write down these currents in the form of an equation. The network equations used are those according to Kirchhoff's laws, and as we are dealing with circuit currents, we will be looking at Kirchhoff's current law, (KCL).

Gustav Kirchhoff's Current Law is one of the fundamental laws used for circuit analysis. His current law states that for a parallel path **the total current entering a circuits junction is exactly equal to the total current leaving the same junction**. This is because it has no other place to go as no charge is lost.

In other words the algebraic sum of ALL the currents entering and leaving a junction must be equal to zero as: $\sum I_{IN} = \sum I_{OUT}$.

This idea by Kirchhoff is commonly known as the **Conservation of Charge**, as the current is conserved around the junction with no loss of current. Lets look at a simple example of Kirchhoff's current law (KCL) when applied to a single junction.

A Single Junction

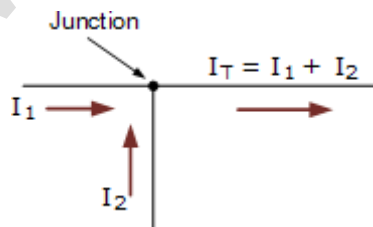

Here in this simple single junction example, the current I_T leaving the junction is the algebraic sum of the two currents, I_1 and I_2 entering the same junction. That is $I_T = I_1 + I_2$.

Note that we could also write this correctly as the algebraic sum of: $I_T - (I_1 + I_2) = 0$.


So if I_1 equals 3 amperes and I_2 is equal to 2 amperes, then the total current, I_T leaving the junction will be $3 + 2 = 5$ amperes, and we can use this basic law for any number of junctions or nodes as the sum of the currents both entering and leaving will be the same.

Also, if we reversed the directions of the currents, the resulting equations would still hold true for I_1 or I_2 . As $I_1 = I_T - I_2 = 5 - 2 = 3$ amps, and $I_2 = I_T - I_1 = 5 - 3 = 2$ amps. Thus we can think of the currents entering the junction as being positive (+), while the ones leaving the junction as being negative (-).

Then we can see that the mathematical sum of the currents either entering or leaving the junction and in whatever direction will always be equal to zero, and this forms the basis of Kirchhoff's Junction Rule, more commonly known as *Kirchhoff's Current Law*, or (KCL).

Resistors in Parallel

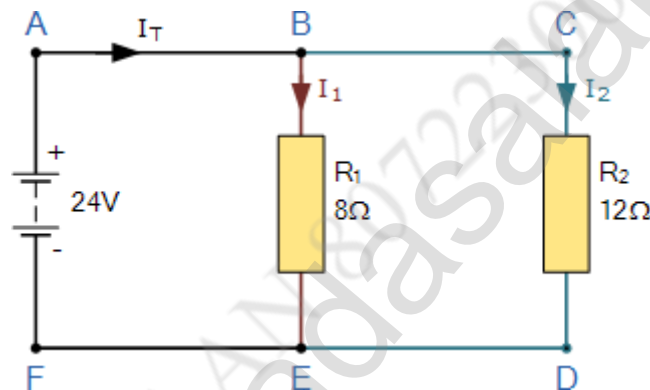Let's look how we could apply Kirchhoff's current law to resistors in parallel, whether the resistances in those branches are equal or unequal. Consider the following circuit diagram:



In this simple parallel resistor example there are two distinct junctions for current. Junction one occurs at node B, and junction two occurs at node E. Thus we can use Kirchhoff's Junction Rule for the electrical currents at both of these two distinct junctions, for those currents entering the junction and for those currents flowing leaving the junction.

To start, all the current, I_T leaves the 24 volt supply and arrives at point A and from there it enters node B. Node B is a junction as the current can now split into two distinct directions, with some of the current flowing downwards and through resistor R_1 with the remainder continuing on through resistor R_2 via node C. Note that the currents flowing into and out of a node point are commonly called branch currents.

We can use Ohm's Law to determine the individual branch currents through each resistor as: $I = V/R$, thus:

For current branch B to E through resistor R_1

$$I_{B-E} = I_1 = \frac{V}{R_1} = \frac{24}{8} = 3A$$

For current branch C to D through resistor R_2

$$I_{C-D} = I_2 = \frac{V}{R_2} = \frac{24}{12} = 2A$$

From above we know that Kirchhoff's current law states that the sum of the currents entering a junction must equal the sum of the currents leaving the junction, and in our simple example above, there is one current, I_T going into the junction at node B and two currents leaving the junction, I_1 and I_2 .

Since we now know from calculation that the currents leaving the junction at node B is I_1 equals 3 amps and I_2 equals 2 amps, the sum of the currents entering the junction at node B must equal $3 + 2 = 5$ amps. Thus $\Sigma_{IN} = I_T = 5$ amperes.

In our example, we have two distinct junctions at node B and node E, thus we can confirm this value for I_T as the two currents recombine again at node E. So, for Kirchhoff's junction rule to hold true, the sum of the currents into point F must equal the sum of the currents flowing out of the junction at node E.

As the two currents entering junction E are 3 amps and 2 amps respectively, the sum of the currents entering point F is therefore: $3 + 2 = 5$ amperes. Thus $\Sigma_{IN} = I_T = 5$ amperes and therefore Kirchhoff's current law holds true as this is the same value as the current leaving point A.

Applying KCL to more complex circuits.

We can use Kirchhoff's current law to find the currents flowing around more complex circuits. We hopefully know by now that the algebraic sum of all the currents at a node (junction point) is equal to zero and with this idea in mind, it is a simple case of determining the currents entering a node and those leaving the node. Consider the circuit below.

Kirchhoff's Current Law Example No1:

In this example there are four distinct junctions for current to either separate or merge together at nodes A, C, E and node F. The supply current I_T separates at node A flowing through resistors R_1 and R_2 , recombining at node C before separating again through resistors R_3 , R_4 and R_5 and finally recombining once again at node F.

But before we can calculate the individual currents flowing through each resistor branch, we must first calculate the circuit's total current, I_T . Ohm's law tells us that $I = V/R$ and as we know the value of V , 132 volts,

Circuit Resistance R_{CF}

$$\frac{1}{R_{(CF)}} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30}$$

$$\frac{1}{R_{(CF)}} = \frac{1}{0.1} \quad \therefore R_{(CF)} = 10\Omega$$


Thus the equivalent circuit resistance between nodes C and F is calculated as 10 Ohms. Then the total circuit current, I_T is given as:

$$R_T = R_{(AC)} + R_{(CF)} = 1 + 10 = 11\Omega$$

$$I_T = \frac{V}{R_T} = \frac{132}{11} = 12 \text{ Amps}$$

Giving us an equivalent circuit of:

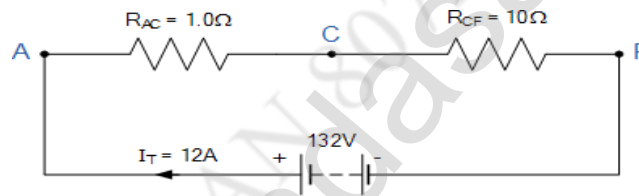Kirchhoff's Current Law Equivalent Circuit



Therefore, $V = 132V$, $R_{AC} = 1\Omega$, $R_{CF} = 10\Omega$'s and $I_T = 12A$.

Having established the equivalent parallel resistances and supply current, we can now calculate the individual branch currents and confirm using Kirchhoff's junction rule as follows.

$$V_{AC} = I_T \times R_{AC} = 12 \times 1 = 12 \text{ Volts}$$

$$V_{CF} = I_T \times R_{CF} = 12 \times 10 = 120 \text{ Volts}$$

$$I_1 = \frac{V_{AC}}{R_1} = \frac{12}{2.4} = 5 \text{ Amps}$$

$$I_2 = \frac{V_{AC}}{R_2} = \frac{12}{1.7} = 7 \text{ Amps}$$

$$I_3 = \frac{V_{CF}}{R_3} = \frac{120}{60} = 2 \text{ Amps}$$

$$I_4 = \frac{V_{CF}}{R_4} = \frac{120}{20} = 6 \text{ Amps}$$

$$I_5 = \frac{V_{CF}}{R_5} = \frac{120}{30} = 4 \text{ Amps}$$

Thus, $I_1 = 5A$, $I_2 = 7A$, $I_3 = 2A$, $I_4 = 6A$, and $I_5 = 4A$.

We can confirm that Kirchoff's current law holds true around the circuit by using node C as our reference point to calculate the currents entering and leaving the junction as:

$$\text{At node C } \sum I_{IN} = \sum I_{OUT}$$

$$I_T = I_1 + I_2 = I_3 + I_4 + I_5$$


$$\therefore 12 = (5 + 7) = (2 + 6 + 4)$$

We can also double check to see if Kirchhoff's Current Law holds true as the currents entering the junction are positive, while the ones leaving the junction are negative, thus the algebraic sum is: $I_1 + I_2 - I_3 - I_4 - I_5 = 0$ which equals $5 + 7 - 2 - 6 - 4 = 0$.

So we can confirm by analysis that Kirchoff's current law (KCL) which states that the algebraic sum of the currents at a junction point in a circuit network is always zero is true and correct in this example.

Kirchoff's Current Law

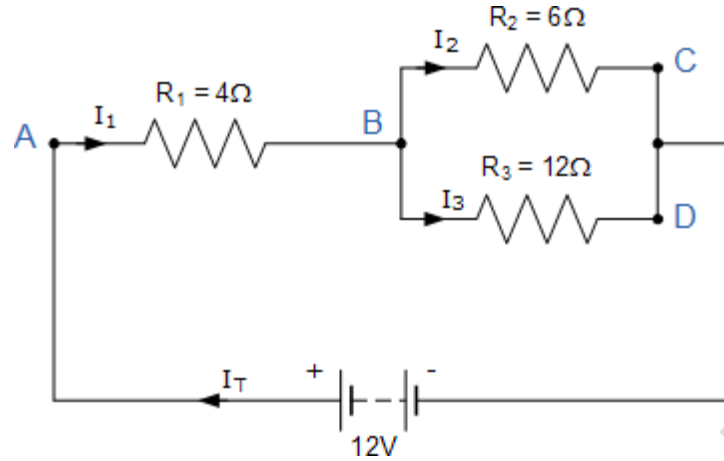Find the currents flowing around the following circuit using Kirchoff's Current Law only.



I_T is the total current flowing around the circuit driven by the 12V supply voltage. At point A, I_1 is equal to I_T , thus there will be an $I_1 \cdot R$ voltage drop across resistor R_1 .

The circuit has 2 branches, 3 nodes (B, C and D) and 2 independent loops, thus the $I \cdot R$ voltage drops around the two loops will be:

- Loop ABC $\Rightarrow 12 = 4I_1 + 6I_2$
- Loop ABD $\Rightarrow 12 = 4I_1 + 12I_3$

Since Kirchoff's current law states that at node B, $I_1 = I_2 + I_3$, we can therefore substitute current I_1 for $(I_2 + I_3)$ in both of the following loop equations and then simplify.

Kirchoff's Loop Equations

| Loop (ABC) | Loop (ABD) |
|----------------------------|-----------------------------|
| $12 = 4I_1 + 6I_2$ | $12 = 4I_1 + 12I_3$ |
| $12 = 4(I_2 + I_3) + 6I_2$ | $12 = 4(I_2 + I_3) + 12I_3$ |
| $12 = 4I_2 + 4I_3 + 6I_2$ | $12 = 4I_2 + 4I_3 + 12I_3$ |
| $12 = 10I_2 + 4I_3$ | $12 = 4I_2 + 16I_3$ |

We now have two simultaneous equations that relate to the currents flowing around the circuit.

Eq. No 1 : $12 = 10I_2 +$

$4I_3$ Eq. No 2 : $12 = 4I_2 + 16I_3$

By multiplying the first equation (Loop ABC) by 4 and subtracting Loop ABD from Loop ABC, we can be reduced both equations to give us the values of I_2 and I_3

$$\begin{aligned} \text{Eq. No 1 : } 12 &= 10I_2 + 4I_3 \quad (\times 4) \quad \Rightarrow 48 = 40I_2 + \\ 16I_3 & \text{Eq. No 2 : } \quad \quad \quad 12 = 4I_2 + 16I_3 \quad (\times 1) \\ \Rightarrow 12 &= 4I_2 + 16I_3 \quad \text{Eq. No 1} - \text{Eq. No 2} \Rightarrow 36 \\ &= 36I_2 + 0 \end{aligned}$$

Substitution of I_2 in terms of I_3 gives us the value of I_2 as 1.0 Amps

Now we can do the same procedure to find the value of I_3 by multiplying the first equation (Loop ABC) by 4 and the second equation (Loop ABD) by 10. Again by subtracting Loop ABC from Loop ABD, we can be reduced both equations to give us the values of I_2 and I_3

$$\begin{aligned} \text{Eq. No 1 : } 12 &= 10I_2 + 4I_3 \quad (\times 4) \quad \Rightarrow 48 = 40I_2 + 16I_3 \quad \text{Eq.} \\ \text{No 2 : } 12 &= 4I_2 + 16I_3 \quad (\times 10) \quad \Rightarrow 120 = 40I_2 + \\ 160I_3 & \text{Eq. No 2} - \text{Eq. No 1} \Rightarrow 72 = 0 + 144I_3 \end{aligned}$$

Thus substitution of I_3 in terms of I_2 gives us the value of I_3 as 0.5 Amps

As Kirchhoff's junction rule states that : $I_1 = I_2 + I_3$

The supply current flowing through resistor R_1 is given as : $1.0 + 0.5 = 1.5$ Amps

Thus $I_1 = I_T = 1.5$ Amps, $I_2 = 1.0$ Amps and $I_3 = 0.5$ Amps and from that information we could calculate the $I \cdot R$ voltage drops across the devices and at the various points (nodes) around the circuit.

We could have solved the circuit of example two simply and easily just using Ohm's Law, but we have used Kirchhoff's Current Law here to show how it is possible to solve more complex circuits when we cannot just simply apply Ohm's Law.

STUDY MATERIALS AVAILABLE

TN-MAWS

(MUNICIPAL ADMINISTRATION & WATER SUPPLY DEPARTMENT)

DEGREE / DIPLOMA:

*** CIVIL / MECHANICAL / EEE / TOWN PLANNING / ARCHITECTURE/ PUBLIC HEALTH AND SANITATION STUDY MATERIALS WITH Q.BANK AVAILABLE.**

INTRODUCTION TO ELECTRICAL CIRCUITS

Circuit concept: Basic definitions, Ohm's law at constant temperature, classifications of elements, R, L, C parameters, independent and dependent sources, Kirchhoff's laws, equivalent resistance of series, parallel and series parallel networks. Star to delta and delta to star transformation, mesh analysis and nodal analysis by Kirchhoff's laws, inspection method, super mesh and super node analysis.

Introduction

The interconnection of various electric elements in a prescribed manner comprises as an electric circuit in order to perform a desired function. The electric elements include controlled and uncontrolled source of energy, resistors, capacitors, inductors, etc. Analysis of electric circuits refers to computations required to determine the unknown quantities such as voltage, current and power associated with one or more elements in the circuit. To contribute to the solution of engineering problems one must acquire the basic knowledge of electric circuit analysis and laws. Many other systems, like mechanical, hydraulic, thermal, magnetic and power system are easy to analyze and model by a circuit. To learn how to analyze the models of these systems, first one needs to learn the techniques of circuit analysis. We shall discuss briefly some of the basic circuit elements and the laws that will help us to develop the background of subject.

Basic electrical circuits use standard symbols for the components in the circuit. Understanding electrical circuits is of great importance nowadays.

As we all know that modern life is overwhelmingly dependent on electricity, it is quite important for people to understand simple electrical circuits. Simple electrical circuits introduction is a good assistant for you to better know electrical circuits.


The Definition of Electrical Circuits

An electrical circuit is a closed loop of conductive material that allows electrons to flow through continuously without beginning or end. There is continuous electrical current goes from the supply to the load in an electrical circuit. People also say that a complete path, typically through conductors such as wires and through circuit elements, is called an electric circuit.

An electrical circuit is an electrical device that provides a path for electrical current to flow. After you get the definition of the electrical circuit, now we are going to show you three simple electrical circuits.

Switch Circuit

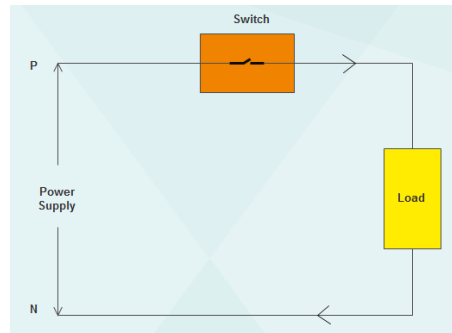
A switch is a device for making and breaking the connection in an electric circuit. We operate switches for lights, fans, electric hair drier and more many times a day but we seldom try to see the connection made inside the switch circuit. The function of the switch is to connect or complete the circuit going to the load from the supply. It has moving contacts which are normally open.



With a switch you can turn the device on or off, therefore, it is a very important component in an electrical circuit.

DC Lighting Circuit

As you can see from the picture below that the LED lamp uses DC supply battery. The battery is bipolar, one is anode and the other is cathode. Moreover, the anode is positive and the cathode is negative. Also, the lamp itself has two ends, one positive and the other is negative. Therefore, the anode of the battery is connected to positive terminal of the lamp, meanwhile the cathode of the battery is connected to the negative terminal of the lamp.

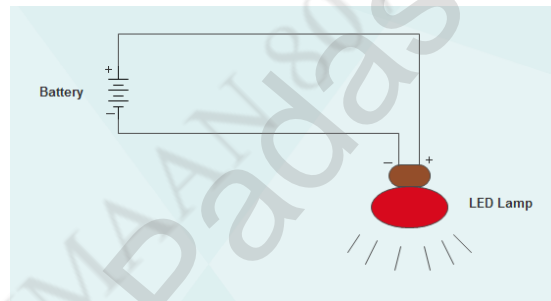

Once the above connection is complete, the LED lamp will light. Although it is simple electrical circuit, many people have no idea how to deal with the connection correctly.

Thermocouple Circuit

If you are looking to build a temperature-sensing device or you need to add sensing capabilities to a large system, you will have to familiarize yourself with thermocouples circuits and understand how to design them. A thermocouple is a device consisting of two dissimilar conductors that contact each other at one or more spots, and it is used to measure temperature. As you can see from the picture below that a thermocouple is made of two wires - iron and constantan, with a voltmeter. If the cold junction temperature is kept constant, then the EMF is proportional to the temperature of the hot junction.



Voltmeter will measure the EMF generated and this can be calibrated to measure the temperature. The temperature difference between the hot and cold junction will produce an EMF proportional to it. Because thermocouple junctions produce such low voltages, it is imperative that wire connections be very clean and tight for accurate and reliable operation. Despite these seemingly restrictive requirements, thermocouples remain one of the most robust and popular methods of industrial temperature measurement in modern use.

A circuit diagram is like a map that shows electricity flows. This tutorial will show you a few of the common symbols and some of the professional terms to help you read circuit diagrams.

Learning to read electrical schematics is like learning to read maps. Electrical schematics show which electrical components used and how they are connected together. The electronic symbols consisted represent each of the components used. The symbols are connected with lines.

Recognizing Electrical Schematic Terms

Here are some of the standard and basic terms of circuit diagrams:


- Voltage: Voltage is the "pressure" or "force" of electricity, it is usually measured in volts (V) and the outlets in common house operate at 120V. Outlets of voltage may differ in other countries.
- Resistance: Resistance represents how easily electrons can flow through a certain material, and it is measured in Ohms (R or Ω). Current flow can move faster in conductors such as gold or copper, in this case we say the resistance is low. The movement of electrons is relatively slow in insulators such as plastic, wood, and air, in this case we say the resistance is high.
- Current: Current is the flow of electricity, or to be more specific, the flow of electrons. Current is measured in Amperes (Amps). The flow of current is only possible when a voltage supply is connected.
- DC (Direct Current): DC is the continuous current flow in one direction. DC can flow not just through conductors, but semi-conductors and insulators too.
- AC (Alternating Current): In AC, the current flow alternates between two directions according to a certain period, it often forms a sine wave. The frequency of AC is measured in Hertz (Hz), and it is usually 60Hz.

Basic Elements & Introductory Concepts

- **Electrical Network:** A combination of various electric elements (Resistor, Inductor, Capacitor, Voltage source, Current source) connected in any manner what so ever is called an electrical network. We may classify circuit elements in two categories, passive and active elements.
- Passive Element: The element which receives energy (or absorbs energy) and then either converts it into heat (R) or stored it in an electric (C) or magnetic (L) field is called passive element.
- Active Element: The elements that supply energy to the circuit is called active element. Examples of active elements include voltage and current sources, generators, and electronic devices that require power supplies. A transistor is an active circuit element, meaning that it can amplify power of a signal. On the other hand, transformer is not an active element because it does not amplify the power level and power remains same both in primary and secondary sides. Transformer is an example of passive element.

* **Bilateral Element:** Conduction of current in both directions in an element (example: Resistance; Inductance; Capacitance) with same magnitude is termed as bilateral element.

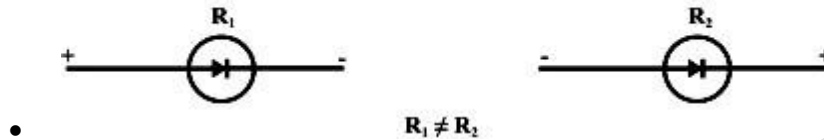- **Unilateral Element:** Conduction of current in one direction is termed as unilateral (example: Diode, Transistor) element.




- **Meaning of Response:** An application of input signal to the system will produce an output signal, the behavior of output signal with time is known as the response of the system.

BASIC CIRCUIT CONCEPTS

An electric circuit is formed by interconnecting components having different electric properties. It is therefore important, in the analysis of electric circuits, to know the properties of the involved components as well as the way the components are connected to form the circuit. In this introductory chapter some ideal electric components and simple connection styles are introduced. Without resort to advanced analysis techniques, we will attempt to solve simple problems involving circuits that contain a relatively small number of components connected in some relatively simple fashions. In particular we will derive a set of useful formulae for dealing with circuits that involve such simple connections as "series", "parallel", "ladder", "star" and "delta". This chapter serves as a review of the basic properties of electric circuits. In addition we will briefly introduce the PSPICE analysis programme and how it can be used to help analyze electric circuits.

Direction and Polarity

Current direction indicates the direction of flow of positive charge, and voltage polarity indicates the relative potential between two points. Usually, "+" is assigned to a higher potential point and "-" to a lower potential point. However, during analysis, direction and polarity can be *arbitrarily* assigned on circuit diagrams. Actual direction and polarity will be governed by the sign of the value. Figure 1.1 shows some examples.

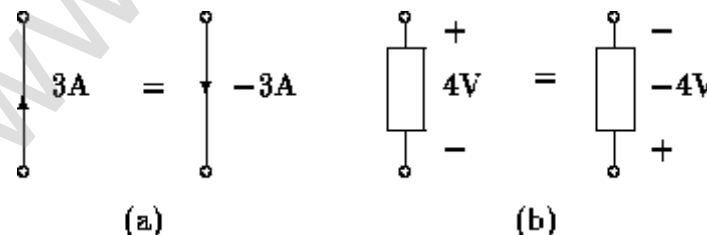

Equivalent assignments of (a) current direction; (b) voltage polarity

Ohm's Law | Equation Formula and Limitation of Ohm's Law

The most basic quantities of electricity are voltage, current and resistance or impedance. **Ohm's law** shows a simple relationship between these three quantities. This law is one of the most basic laws of electricity.

This law helps to calculate the power, efficiency, current, voltage and resistance or impedance of any element of electrical circuit.

Statement of Ohm's Law:

Whenever, we apply a potential difference i.e. voltage across a resistor of a closed electric circuit, current starts flowing through it. The statement of Ohm's law says that The current (I) is directly proportional to the applied voltage (V), provided temperature and all other factors remain constant.

Mathematically, $I \propto V$ i.e. $V \propto I \Rightarrow V = RI$

Where, R is constant of proportionality.

This equation presents the statement of Ohm's law. Here, we measure current in Ampere (or amps), voltage in unit of volt. The constant of proportionality R is the property of the conductor; we know it as resistance and measure it in ohm (Ω). Theoretically, the resistance has no dependence on the applied voltage, or on the flow of current. The value of R changes only if the conditions (like temperature, diameter and length etc.) of the resistor are changed by any means.

History of Ohm's Law

In the month of May 1827, Georg Simon Ohm published a book "Die GalvanischeKette, MathematischBearbeitet". "Die GalvanischeKette, MathematischBearbeitet" means "The Galvanic Circuit Investigated Mathematically". He presented the relationship between voltage (V), current (I), and resistance (R) based on his experimental data, in this book. Georg Simon Ohm had defined the fundamental interrelationship between current, voltage and resistance of a circuit which was later named Ohm's law. Because of this law and his excellence in the field of science and academics, he got the Copley Medal award in 1841. In 1872 the unit of electrical resistance was named 'OHM' in his honor.

Ohm's Law Physics

We can understand the physics behind Ohm's law well if we examine it from atomic level of a metal. A metal conductor contains plenty of free electrons. These free electrons randomly move in the conductor. When, we apply a voltage, across the conductor, the free electrons keep being accelerated towards higher potential end due to electrostatic force of the applied voltage. This means they acquire some kinetic energy as they move towards the + Ve end of the conductor. However, before they get very far they collide with an atom or ion, lose some of their kinetic energy and may bounce back. Again due to presence of static electric field the free electrons again being accelerated. This keeps happening. That means, even after application of external electric field, there will be still random motion in the free electrons of the conductor. Each free electron drifts towards +Ve end with its inherent random motion. As a result, the free electrons tend to "drift" towards the + Ve end, bouncing around from atom to atom on the way. This is how the materials resist a current. If we apply more voltage across the conductor, the more free electrons will move with more acceleration which causes more drift velocity of the electrons. The drift velocity of the electrons is proportional to the applied static electric field. That more electrons pass through a cross section per unit time, which means more charge transfer per unit time. The rate of charge transfer per unit time is current.

Applications of Ohm's Law


The **applications of ohm's law** are that it helps us in determining either voltage, current or impedance or resistance of a linear electric circuit when the other two quantities are known to us. Apart from that, it makes power calculation a lot simpler, like when we know the value of the resistance for a particular circuit element, we need not know both the current and the voltage to calculate the power

$$V = RI \Rightarrow I = \frac{V}{R}$$

dissipation since, $P = VI$.

To replace either the voltage or current in the above expression to produce the result
 Thus, $P = VI = \frac{V^2}{R} = I^2R$ (Since $V = IR$)

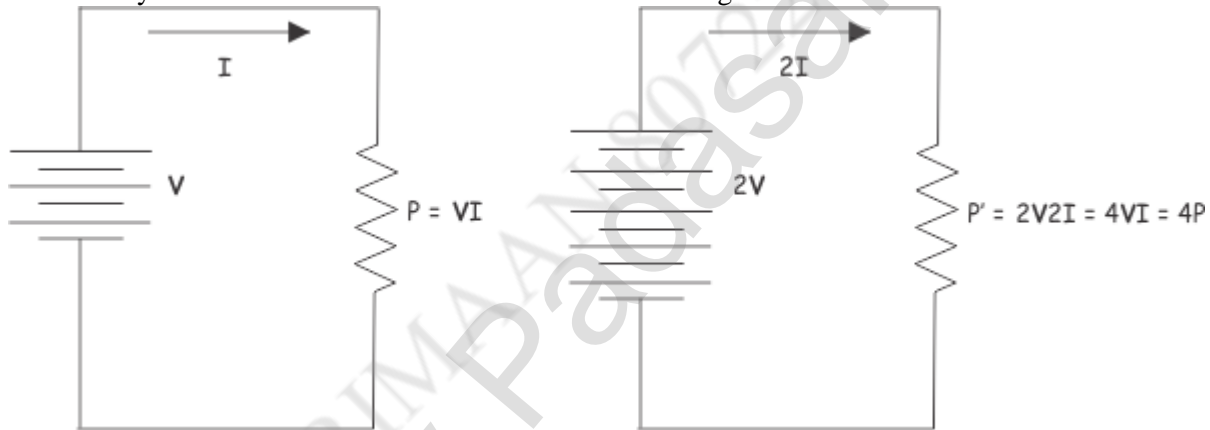We can see from the results, that the rate of energy loss varies with the square of the voltage or current. When we double the voltage applied to a circuit, obeying Ohm's law, the rate at which energy is supplied (or power) gets four times bigger. Similarly, the power dissipation at a circuit element is increased by 4 times when we make double the current through it.



Limitation of Ohm's Law

The **limitations of Ohm's law** are explained as follows:

1. This law cannot be applied to unilateral networks. A unilateral network has unilateral elements like diode, transistors, etc., which do not have same voltage current relation for both directions of current.
2. **Ohm's law** is also not applicable for non – linearelements.

Non-linear elements are those which do not have current exactly proportional to the applied voltage, that means the resistance value of those elements changes for different values of voltage and current. Examples of non – linear elements are thyristor, electric arc, etc.

Mesh and Nodal Analysis

MESH ANALYSIS

Mesh analysis is a technique used to solve the complex networks consisting of more number of meshes.

Mesh analysis is nothing but applying KVL to each and every loop in circuit and solving for mesh currents. By finding the mesh currents we can solve any require data of the network.

Let $V_1 = 30v$, $V_2 = 40v$, $R_1 = 4$ ohms, $R_2 = 2$ ohms and $R_3 = 4$ ohms

i_1, i_2 are the mesh currents, here positive direction of currents are assumed, but in general we can assume current directions in any fashion and can solve.

Applying KVL to first loop we get, $V_1 - i_1R_1 - (i_1+i_2)R_2$.

$$V_1 = (R_1+R_2)i_1 + i_2.R_2. \text{----- } 1$$

Applying KVL to second loop we get, $V_2 - i_2R_3 - (i_1+i_2)R_2$.

$$V_2 = (R_1+R_2)i_1 + i_2.R_3. \text{----- } 2$$

Hence by solving eq. 1 and 2 we can get mesh currents i_1 and i_2 .

Mesh analysis by inspection method:

Inspection method is direct method using mesh currents can be find directly without applying KVL. Let us take same network as above, representing eq 1 and 2 in matrix form.

To be continued.....

STUDY MATERIALS AVAILABLE

TN-MAWS

(MUNICIPAL ADMINISTRATION & WATER SUPPLY DEPARTMENT)

DEGREE / DIPLOMA:

*** CIVIL / MECHANICAL / EEE / TOWN PLANNING / ARCHITECTURE/ PUBLIC HEALTH AND SANITATION STUDY MATERIALS WITH Q.BANK AVAILABLE.**

SRIMAAN COACHING CENTRE-TRICHY.

TO CONTACT:8072230063.

SRIMAAN COACHING CENTRE-TRICHY: TET/PG-TRB / UG-TRB
BEO/ DEO/TRB-POLY/ASST.PROF/COM.INS/TNEB/SCERT/JSO
STUDY MATERIALS AVAILABLE- CONTACT:8072230063.

2024-25
SRIMAAN

UG-TRB MATERIALS

GRADUATE TEACHERS / BLOCK RESOURCE TEACHER EDUCATORS (BRTE) & SGT

- UG TRB: TAMIL MATERIAL WITH QUESTION BANK.
- UG TRB: ENGLISH STUDY MATERIAL +Q. BANK.
- UG-TRB: MATHEMATICS MATERIAL WITH Q. BANK (E/M)
- UG TRB: PHYSICS MATERIAL WITH QUESTION BANK (E/M)
- UG TRB: CHEMISTRY MATERIAL + QUESTION BANK (E/M)
- UG TRB: HISTORY MATERIAL + Q.BANK (E/M)
- UG TRB: ZOOLOGY MATERIAL + QUESTION BANK (E/M)
- UG TRB: BOTANY MATERIAL +QUESTION BANK (T/M& E/M)
- UG TRB: GEOGRAPHY STUDY MATERIAL (E/M)

SCERT/DIET/GTTI (LECTURER) STUDY MATERIAL AVAILABLE.

TRB-POLYTECHNIC LECTURER-(NEW SYLLABUS) STUDY MATERIALS AVAILABLE

- MATHEMATICS STUDY MATERIAL with Question Bank.
- ENGLISH STUDY MATERIAL with Question Bank.
- PHYSICS STUDY MATERIAL with Question Bank.

kindly send me your key answers to our email id - padasalai.net@gmail.com22

- **CHEMISTRY STUDY MATERIAL with Question Bank.**
- **MODERN OFFICE PRACTICE STUDY MATERIAL with Q.B.**
- **COMPUTER SCIENCE STUDY MATERIAL with Question Bank.**
- **INFORMATION TECHNOLOGY STUDY MATERIAL with Q.Bank.**
- **ECE STUDY MATERIAL with Question Bank.**
- **EEE STUDY MATERIAL With Question Bank.**
- **MECHANICAL STUDY MATERIAL With Question Bank.**
- **CIVIL STUDY MATERIAL With Question Bank.**
- **EIE STUDY MATERIAL with Question Bank.**
- **ICE STUDY MATERIAL with Question Bank.**

PG-TRB MATERIALS

- **PG TRB: TAMIL STUDY MATERIAL +QUESTION BANK (T/M)**
- **PG TRB: ENGLISH MATERIAL WITH QUESTION BANK.**
- **PG-TRB: MATHEMATICS MATERIAL WITH Q.BANK (E/M)**
- **PG TRB: PHYSICS MATERIAL WITH QUESTION BANK (E/M)**
- **PG TRB: CHEMISTRY MATERIAL + QUESTION BANK (E/M)**
- **PG TRB: COMMERCE MATERIAL WITH Q.BANK (T/M)&(E/M)**
- **PG TRB:ECONOMICS MATERIAL+Q. BANK (T/M & E/M)**

**SRIMAAN COACHING CENTRE-TRICHY: TET/PG-TRB / UG-TRB
BEO/ DEO/TRB-POLY/ASST.PROF/COM.INS/TNEB/SCERT/JSO
STUDY MATERIALS AVAILABLE- CONTACT:8072230063.**

**2024-25
SRIMAAN**

- **PG TRB: HISTORY MATERIAL + Q. BANK (T/M & E/M)**
- **PG TRB: ZOOLOGY MATERIAL + QUESTION BANK (E/M)**
- **PG TRB: BOTANY MATERIAL +QUESTION BANK (T/M& E/M)**
- **PG TRB: GEOGRAPHY STUDY MATERIAL (E/M)**

**TN-MAWS-MUNICIPAL ADMINISTRATION & WATER SUPPLY
DEPARTMENT-STUDY MATERIALS AVAILABLE.**

TNPSC-(CESE)-JSO STUDY MATERIAL AVAILABLE.

**PG-TRB: COMPUTER INSTRUCTOR-GRADE-I (NEW SYLLABUS)-
2024-2025 STUDY MATERIAL WITH Q.BANK AVAILABLE**

**TNPSC-DEO (District Educational Officer(Group – I C Services)
(TAMIL & ENGLISH MEDIUM) STUDY MATERIAL AVAILABLE.**

**TRB-BEO (Block Educational Officer)
(TAMIL & ENGLISH MEDIUM) STUDY MATERIAL AVAILABLE.**

**TRB-ASSISTANT PROFESSORS IN GOVERNMENT ARTS AND SCIENCE
COLLEGES & COLLEGES OF EDUCATION STUDY MATERIALS AVAILABLE.**

TANGEDCO (TNEB)-(T/M & E/M)

ASSESSOR/ASSISTANT ENGINEER (A.E)/JUNIOR ASSISTANT (ACCOUNTS)

10% Discount for all materials. Materials are sending through

COURIER.

TO CONTACT

8072230063

SRIMAAN

kindly send me your key answers to our email id - padasalai.net@gmail.com24