
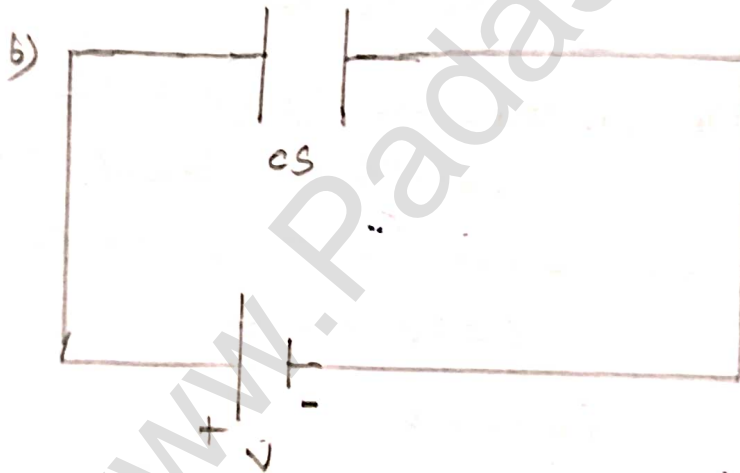


20)

3 mark

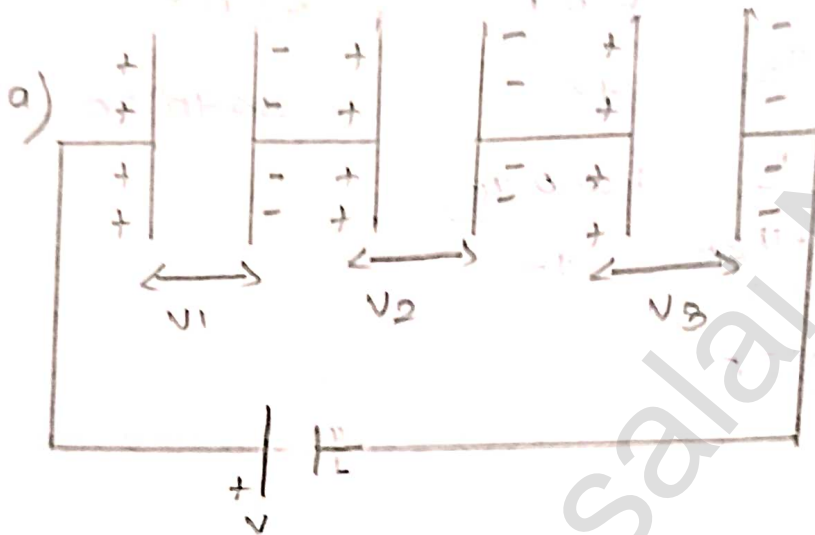1) capacitor series connection (or) Parallel Plate That

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



$$V = V_1 + V_2 + V_3$$

$V \rightarrow$  Potential difference

$$C = \frac{Q}{V}$$

$$V = \frac{Q}{C}$$

$$V_1 = \frac{Q}{C_1} \rightarrow \text{①}$$

$$V_2 = \frac{Q}{C_2} \rightarrow (2)$$

$$V_3 = \frac{Q}{C_3} \rightarrow (3)$$

Total potential difference

$$V = V_1 + V_2 + V_3$$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$V = \frac{Q}{C}$$

$$C = C_3$$

$$\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$


$$\frac{Q}{C} = Q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

This equivalent capacitance  $C$  is always less than the smallest individual capacitance in the series

capacitance in parallel connection <sup>(or)</sup> prove that

$$C_p = C_1 + C_2 + C_3$$

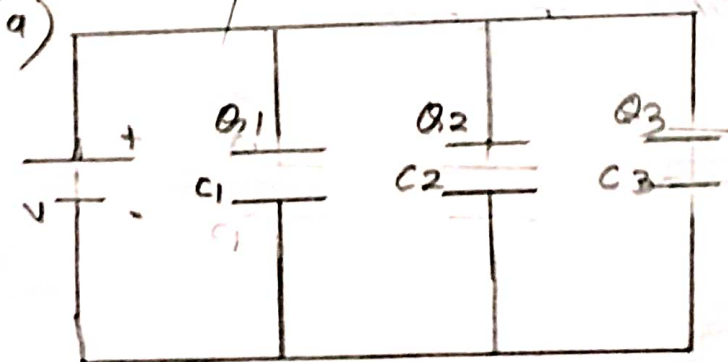

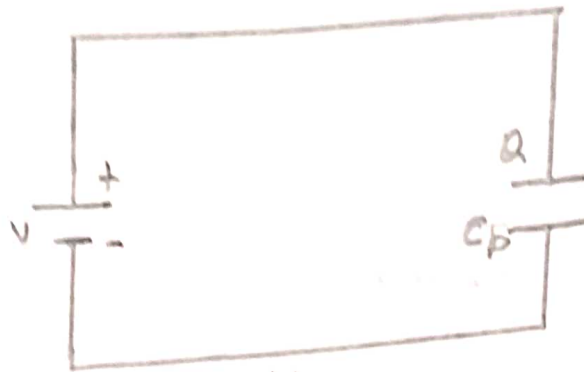

b)

$$Q = Q_1 + Q_2 + Q_3$$

$$C = Q/V$$

$$Q = CV$$

$$Q_1 = C_1 V \rightarrow ①$$

$$Q_2 = C_2 V \rightarrow ②$$

$$Q_3 = C_3 V \rightarrow ③$$

$$CV = C_1 V + C_2 V + C_3 V$$

$$C = C_p$$

$$C_p V = C_1 V + C_2 V + C_3 V$$

$$C_p V = V(C_1 + C_2 + C_3)$$

$$C_p = C_1 + C_2 + C_3$$

In a parallel connection it is equivalent as area of each capacitance adds to give more effective area such that total capacitance increases

2)  $2\mu f$ ,  $2\mu f$ ,  $2\mu f$  series and parallel connection

$$C_1 = 2\mu f$$

$$C_2 = 2\mu f$$

$$C_3 = 2\mu f$$

series connection

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_s} = \frac{1}{2} + \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{C_s} = \frac{1+1+1}{2}$$

$$\frac{1}{C_s} = \frac{3}{2}$$

$$\frac{1}{C_s} = \frac{2}{3} \mu f \quad (\text{or})$$

$$C_s = \left(\frac{2}{3}\right) \times 10^{-6} f$$

parallel connection

$$C_p = C_1 + C_2 + C_3 = 2 + 2 + 2$$

$$= 6\mu f$$

$$= 6 \times 10^{-6} f$$

3)  $9\mu f$ ,  $9\mu f$ ,  $9\mu f$  series and parallel connection

series:

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_s} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

Dr. G. THIRUMOORTHY, M.Sc., B.Ed., Ph.D.,  
Guest Lecturer  
PG and Research Department of Physics  
Government Arts College (Autonomous)  
SALEM - 636 007.

8610560810

$$\frac{1}{C_s} = \frac{1+1+1}{9}$$

$$\frac{1}{C_s} = \frac{3}{9}$$

$$C_s = 9/3 = \frac{3 \times 3}{3}$$

$$= 3 \mu\text{f}$$

$$C_s = 3 \times 10^{-12} \text{ f}$$

Parallel connection

$$C_p = C_1 + C_2 + C_3$$

$$C_p = 9 + 9 + 9$$

$$C_p = 27 \mu\text{f}$$

(29)

$$C_p = 27 \times 10^{-12} \text{ f}$$

4)  $2 \mu\text{f}$   $14 \mu\text{f}$  series and parallel connection

series connection

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_s} = \frac{1}{2} + \frac{1}{4}$$

$$\frac{1}{C_s} = \left( \frac{2 \times 1}{2 \times 2} \right) + \frac{1 \times 1}{1 \times 4}$$

$$\frac{1}{C_s} = \frac{2}{4} + \frac{1}{4}$$

$$\frac{1}{C_s} = \frac{2+1}{4}$$

(Q9)

$$C_s = 4/3 \times 10^{-6} f$$

Parallel connection

$$C_p = C_1 + C_2$$

$$C_p = 2 + 4$$



$$= 6 \mu f$$

$$= 6 \times 10^{-6} f.$$

Pg: 77

Exercise problem

11)

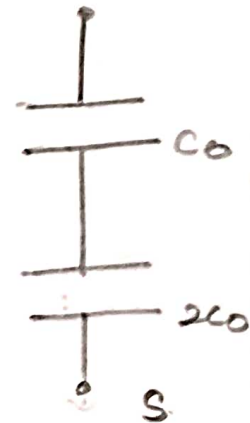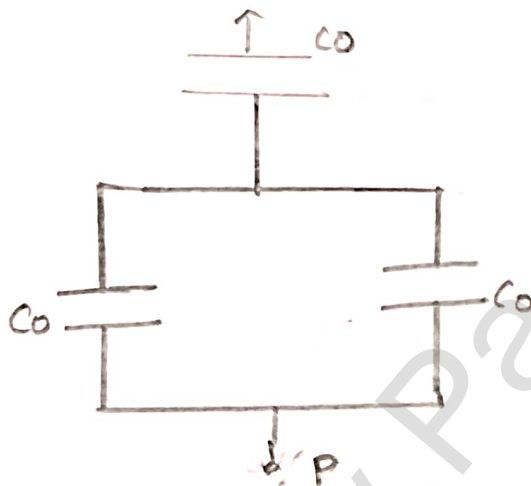

Parallel connection

$$C_p = C_1 + C_2$$

$$C_p = C_0 + C_0$$

$$C_1 = 2C_0$$

series connection

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_0} = \frac{1}{C_0} + \frac{1}{2C_0}$$

$$\frac{1}{C_S} = \left( \frac{2 \times 1}{2 \times C_0} \right) + \left( \frac{1 \times 1}{1 \times 2 \times C_0} \right)$$



$$\frac{1}{C_S} = \frac{2}{2C_0} + \frac{1}{2C_0}$$

$$\frac{1}{C_S} = \frac{2+1}{2C_0}$$

$$\frac{1}{C_S} = \frac{3}{2C_0}$$

$$C_S = \frac{2}{3} C_0$$

ii)

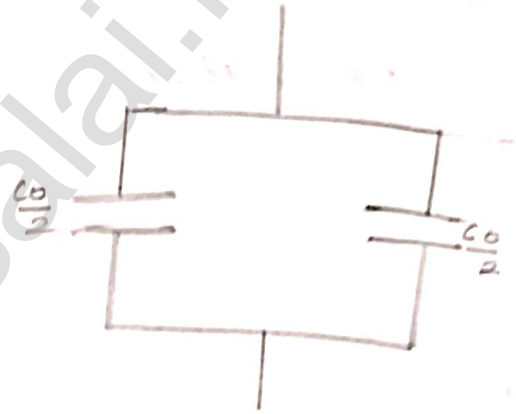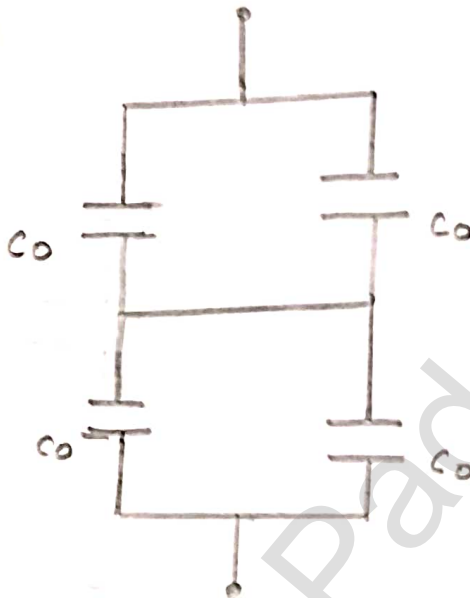

series

$$\frac{1}{C_{S1}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{S1}} = \frac{1}{C_0} + \frac{1}{C_0}$$

$$\frac{1}{C_{S1}} = \frac{1+1}{C_0} = \frac{2}{C_0}$$

$$C_S = \frac{C_0}{2} \rightarrow \textcircled{1}$$

$$\frac{1}{C_{S2}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{S2}} = \frac{1}{C_0} + \frac{1}{C_0}$$

$$\frac{1}{C_{S2}} = \frac{1+1}{C_0}$$

$$\frac{1}{C_{S2}} = \frac{2}{C_0}$$

$$C_{S2} = \frac{C_0}{2} \rightarrow \textcircled{B}$$

$$C_1 = \frac{C_0}{2}$$

$$C_2 = \frac{2}{C_0}$$

$$C_p = C_1 + C_2$$


$$C_p = \frac{C_0}{2} + \frac{C_0}{2}$$

$$C_p = \frac{2C_0}{2}$$

$$C_p = C_0$$

Dr. G. THIRUMORTHY, M.Sc. B.Ed. Ph.D.  
 Guest Lecturer  
 PG and Research Department of Physics  
 Government Arts College (Autonomous)  
 SALEM - 636 007.  
 8610560810


ii)

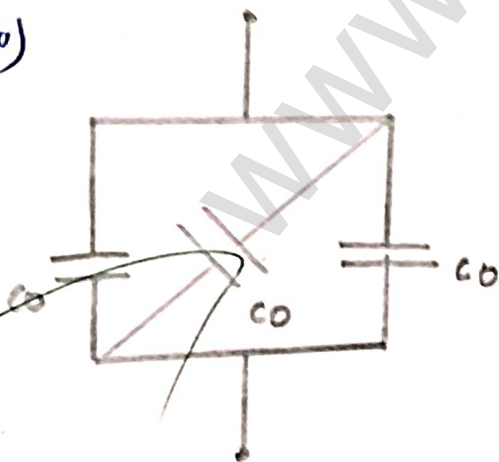

$$C_p = C_1 + C_2 + C_3$$

$$C_p = C_0 + C_0 + C_0$$



$$C_p = 3C_0$$

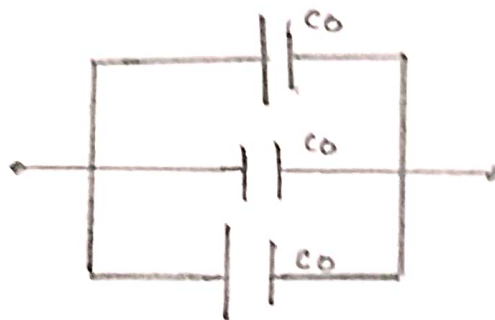



Pg: 73.  
 1 mark  
 (4) (17)

(iv)

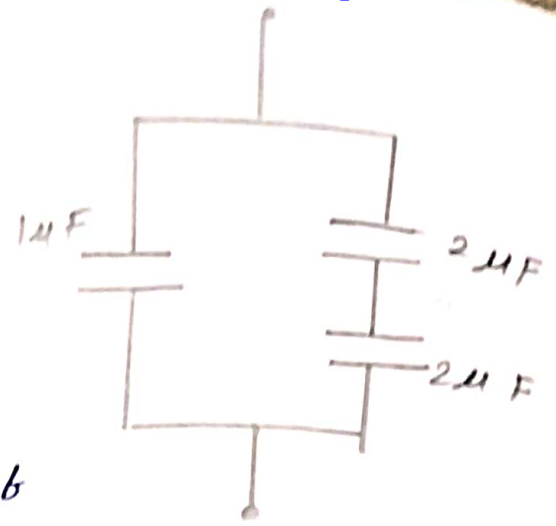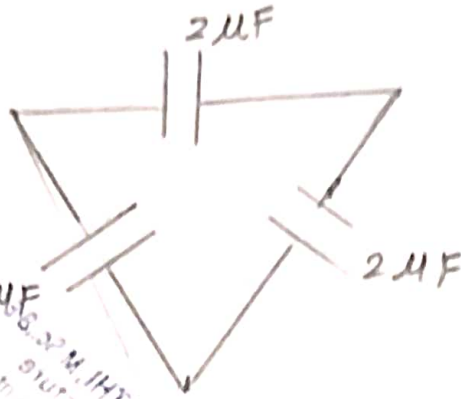

ii)  $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$   
 $C_1 = 2 \mu f$   
 $C_2 = 2 \mu f$

$\frac{1}{C_s} = \frac{1}{2} + \frac{1}{2} = \frac{1+1}{2}$


$\frac{1}{C_s} = \frac{2}{2} = 1$

$C_s = 1 \mu f = 1 \times 10^{-6} f$

iii)  $C_p = C_1 + C_2$

$C_1 = 1 + 1$

$C_1 = 2 \mu f = 2 \times 10^{-6} f$

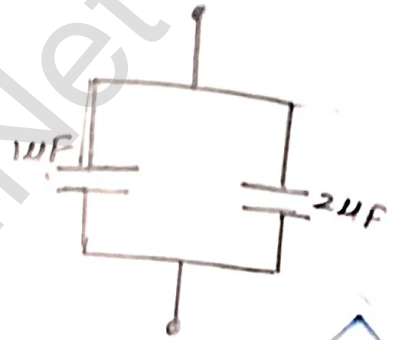

Dr. G. THIRUMURTHY, M.Sc. B.Ed. Ph.D.,  
 Guest Lecturer  
 PG and Research Department of Physics  
 Government Arts College (Autonomous)  
 SALEM - 636 007.  
 8610560810

Q.2  
 11/11/2024