

Example 2.10

Two resistors when connected in series and parallel, their equivalent resistances are $15\ \Omega$ and $\frac{56}{15}\ \Omega$ respectively. Find the values of the resistances

Solution :

$$\text{Series connection} = 15\ \Omega$$

$$\text{Parallel connection} = \frac{56}{15}\ \Omega$$

$$R_s = R_1 + R_2 = 15\ \Omega \rightarrow \textcircled{1}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{56}{15}\ \Omega \rightarrow \textcircled{2}$$

$$\frac{1}{R_p} = \frac{R_1 + R_2}{R_1 R_2} = \frac{56}{15}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{56}{15} \rightarrow \textcircled{3}$$

$$R_p = \frac{R_1 R_2}{15} = \frac{56}{15}$$

$$\frac{R_1 R_2}{15} = \frac{56}{15}$$

$$R_1 R_2 = \frac{56}{15} \times 15$$

$$R_1 R_2 = 56$$

$$R_2 = \frac{56}{R_1} \rightarrow \textcircled{4}$$

From equation (1)

$$R_2 = \frac{56}{R_1}\ \Omega$$

From equation 1

$$R_1 + R_2 = 15\ \Omega$$

$$R_1 + \frac{56}{R_1} = 15$$

$$\frac{R_1(R_1) + 56}{R_1} = 15$$

$$\frac{R_1^2 + 5b}{R_1} = 15$$

$$R_1^2 + 5b = 15R_1$$

$$R_1^2 + 5b - 15R_1 = 0$$

$$R_1^2 - 15R_1 + 5b = 0 \rightarrow (5)$$

factorization method

$$(R_1 - 8)(R_1 - 7) = 0$$

$$(R_1 - 8)(R_1 - 7) = 0$$

$$R_1 - 8 = 0$$

$$R_1 = 8 \Omega$$

From (5) equation

$$R_1 + R_2 = 15 \Omega$$

$$R_1 = 8 \Omega$$

$$8 + R_2 = 15$$

$$R_2 = 15 - 8$$

$$R_2 = 7 \Omega$$

$$R_2 - 7 = 0$$

$$R_2 = 7 \Omega$$

$$R_1 = 7 \Omega$$

$$R_1 + R_2 = 15 \Omega$$

$$7 + R_2 = 15$$

$$R_2 = 15 - 7$$

$$R_2 = 8 \Omega$$

colour coding for Resistor

colour	number	multiplier	Tolerance
Black	0	1	
Brown	1	10^1	
Red	2	10^2	
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	
Blue	6	10^6	
Violet	7	10^7	

gray	8	108	
white	9	109	
gold		10^{-1}	5%
silver		10^{-2}	10%
colourless			20%

Resistor colour code

3 colour

Tolerance → ③



Gold = 5%

Silver = 10%

Colourless = 20%

2 mark

- 1) green
- 2) blue
- 3) orange

Gold 55000

Tolerance 55 × 1000

55×10^3

$55 \text{ K} \Omega \pm 5\%$

Book
Back

- 1) Green, Blue, orange, gold tolerance

$56000 \pm 5\%$

$56 \times 1000 \pm 5\%$

$56 \times 10^3 \pm 5\%$

$56 \text{ K} \Omega \pm 5\%$

$10^{-3} \rightarrow$ kilo

$10^{-3} \rightarrow$ milli

2) orange, orange, orange, gold tolerance

$$33000 \pm 5\%$$

$$33 \times 1000 \pm 5\%$$

$$33 \times 10^3 \pm 5\%$$

$$33 \text{ K} \Omega \pm 5\%$$

3) yellow, violet, orange - silver

$$47000 \pm 10\%$$

$$47 \times 1000 \pm 10\%$$

$$47 \times 10^3 \pm 10\%$$

$$47 \text{ K} \Omega \pm 10\%$$

$$\text{yellow} = 4$$

$$\text{violet} = 7$$

$$\text{orange} = 3$$

$$\text{silver} = 10\%$$

Book
Book
0 mark

4) yellow - green - violet - gold

$$450000000$$

$$45 \times 10000000$$

$$45 \times 10^7 \pm 5\%$$

5) Brown, Black, orange, colourless

$$10000$$

$$10 \times 1000 \pm 20\%$$

$$10 \times 10^3 \pm 20\%$$

$$10 \text{ K} \Omega \pm 20\%$$

$$\text{Brown} = 1$$

$$\text{Black} = 0$$

$$\text{orange} = 3$$

$$\text{colourless} = 20\%$$

6) white, gray, orange, gold - T

$$98000 \pm 5\%$$

$$98 \times 1000 \pm 5\%$$

$$98 \times 10^3 \pm 5\%$$

$$98 \text{ K} \Omega \pm 5\%$$

$$\text{white} = 9$$

$$\text{gray} = 8$$

$$\text{orange} = 3$$

$$\text{gold} = 5\%$$

3 mark

5) Brown, Black, yellow

- a) $100k\Omega$
- b) $10k\Omega$
- c) $1k\Omega$
- d) $1000k\Omega$

Brown = 1 Black = 0 yellow = 4

100000
 100×10^3
 $100k\Omega$

8) Brown, Black, orange

- a) $100k\Omega$
- b) $10k\Omega$
- c) $1k\Omega$
- d) $1000k\Omega$



10000
 10×1000
 10×10^3
 $10k\Omega$

Brown = 1
 Black = 0
 orange = 3

9) Red - Red - Black

- a) 2.2Ω
- b) 22Ω
- c) 2202.2Ω
- d) $2.2k\Omega$

22×1
 22Ω

Joules' law (or) Heating law

$$H = I^2 R t$$

$\frac{t}{1}$ → Time period

H → Heat

t → taken time

I → current

R → Resistance

t → taken time

Example 2.27

Find the heat energy produced in a resistance of 10Ω when 5 A current flows through it for 5 minutes

3 mark

DR. G. THIRUMOGAI, M.Sc. B.Ed., P.H.D.
 Guest Lecturer
 PG and Research Department of Physics
 Government Arts College (Autonomous)
 EM - 636 001

$$R = 10 \Omega$$

$$I = 5 A$$

$$t = 5 \text{ minutes} = 5 \times 60 = 300 \text{ seconds}$$

$$H = ?$$

$$H = I^2 R t$$

$$H = (5)^2 \times 10 \times 5 \times 60$$

$$H = 25 \times 10 \times 300$$

$$H = 250 \times 300$$

$$H = 75000 J$$

$$H = 75 \times 1000$$

$$H = 75 \times 10^3$$

$$H = 75 kJ$$

2) Creative Question

$$R = 10 \Omega$$

$$I = 5 A$$

$$t = 5 \text{ second}$$

$$H = ?$$

$$H = I^2 R t$$

$$H = (5)^2 \times 10 \times 5$$

$$H = 25 \times 10 \times 5$$

$$H = 25 \times 50$$

$$H = 1250 J$$

Q. 2
21/09/24

Dr. G. THIRUMOORTHY, M.Sc., B.Ed., Ph.D.,
Guest Lecture
PG and Research Department of Physics
Government Arts College (Autonomous)
SALEM - 636 007.
8610 560210

22/11/24
Mondaycurrent density

current density - J

$$J = \frac{I}{A}$$

$$I = Q/t$$

J → current density

I → current

A → cross sectional area

$$J = \frac{I}{A} = \frac{A}{m^2}$$

$$= \underline{A m^{-2}}$$

current density : vector quantity

IM

current : scalar quantity

Resistivity (Ω m)

$$R = \frac{l}{\sigma A} \rightarrow \textcircled{1}$$

unit: Ω m

R → Resistance

l → length of the wire

σ → conductivity

A → cross sectional area

σ → conductivity

ρ → Resistivity

$$\rho = \frac{1}{\sigma} \rightarrow \textcircled{2}$$

From equation ①

$$R = \frac{l}{\sigma A}$$

$$R = \frac{1}{\sigma} \left(\frac{l}{A} \right)$$

Dr. G. THIRUMOORTHY, M.Sc., B.Ed., Ph.D.,
 Guest Lecture
 PG and Research Department of Physics
 Government Arts College (Autonomous)
 SALEM - 636 007.

86 56 88 10

$$l = 1m$$

$$A = 1m^2$$




$$R = \rho \rightarrow \textcircled{4}$$

20K
Balt

Pg: 120

L/A

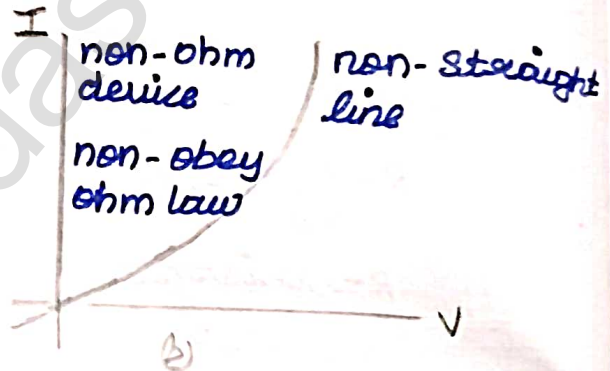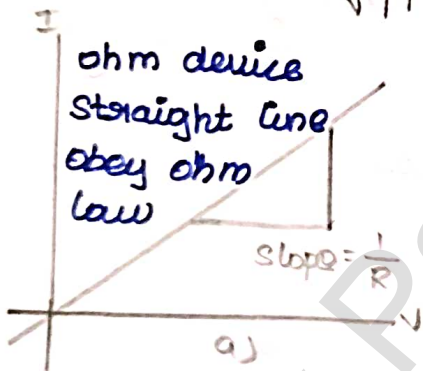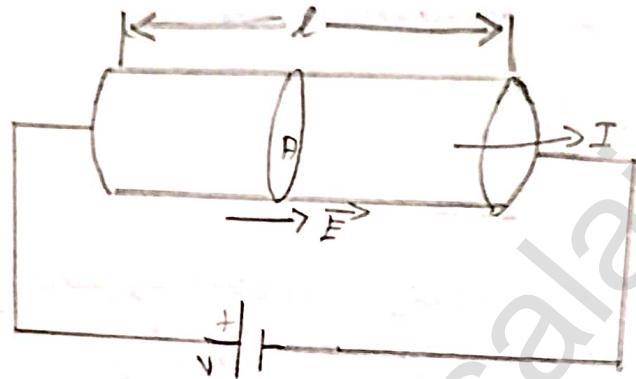2) obtain the microscopic form of Ohm's law from its microscopic form and discuss its limitation



$$\boxed{J = \sigma E} \rightarrow \textcircled{1}$$

J → current density

$$J = I/A$$

σ → conductivity

E → Electric field

$$\boxed{V = E l} \rightarrow \textcircled{2}$$

V → potential difference

E → Electric field

l → length of the conductivity

$$V = E l$$

$$\boxed{E = V/l} \rightarrow \textcircled{3}$$

From equation ①

$$J = \sigma E$$

$$J = \sigma \left(\frac{V}{l} \right)$$

$$J = \frac{I}{A}$$

$$\frac{I}{A} = J \left(\frac{V}{l} \right) \rightarrow \text{④}$$

$$\frac{I l}{A} = \sigma (V)$$

$$\frac{I l}{\sigma A} = V$$

$$V = I \left(\frac{l}{\sigma A} \right)$$

$$V = I R \rightarrow \text{⑤}$$

$$R = \frac{V}{I} \rightarrow \text{⑥}$$

Pg: 39

5 mark

Example 2.6

The resistance of a wire is 20Ω what will be new resistance if it is stretched uniformly 8 times its original length?

$$R_1 = 20 \Omega \quad R_2 = ?$$

$$R = \rho \frac{l}{A}$$

$$R_1 = \rho \frac{l_1}{A_1} \rightarrow \text{①}$$

$$R_2 = \rho \frac{l_2}{A_2} \rightarrow \text{②}$$

$$R_2 = \rho \frac{8l}{A_2} \rightarrow \text{③}$$

$$\frac{R_2}{R_1} = \frac{\rho \frac{8l}{A_2}}{\rho \frac{l_1}{A_1}}$$

$$\frac{R_2}{R_1} = \frac{8l}{\frac{A_2}{\frac{l_1}{A_1}}}$$

$$\frac{R_2}{R_1} = \frac{8l}{A_2} \times \frac{A_1}{l_1}$$

$$l_1 = l$$

$$\frac{R_2}{R_1} = \frac{8l}{A_2} \times \frac{A_1}{l}$$

$$\frac{R_2}{R_1} = \frac{8l}{l} \times \frac{A_1}{A_2}$$

$$\frac{R_2}{R_1} = \frac{A_1}{A_2} \times 8 \rightarrow (4)$$

Initial volume = Final volume

$$A_1 l_1 = A_2 l_2$$

$$l_1 = l \quad l_2 = 8l$$

$$A_1 l = A_2 8l$$

$$\frac{A_1}{A_2} = 8 \rightarrow (5)$$

From equation (4)

$$\frac{R_2}{R_1} = \frac{A_1}{A_2} \times 8$$

$$= 8 \times 8$$

$$\frac{R_2}{R_1} = 64$$

$$R_2 = 64 \times R_1$$

$$R_2 = 64 \times 20$$


$$R_2 = 1280 \Omega$$

28/4/24
Tuesday

PG: 120

11A


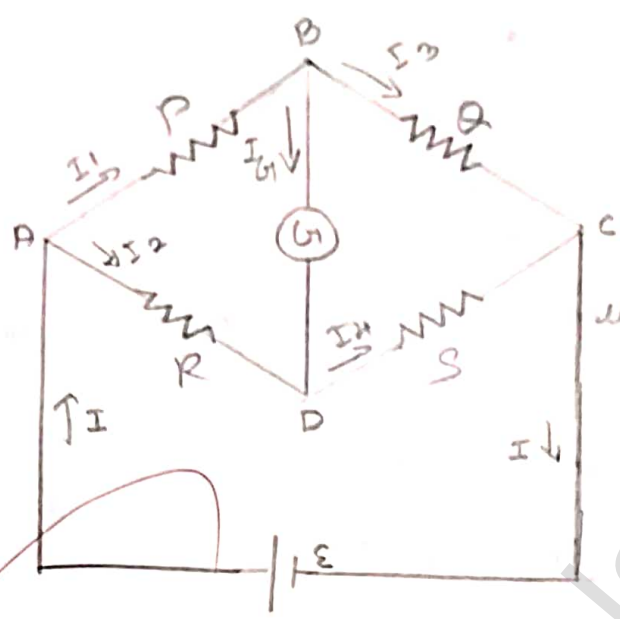
Obtain the condition for bridge balance in wheatstone's bridge



wheatstone's bridge

Kirchhoff's rule

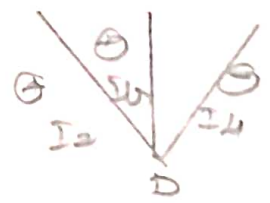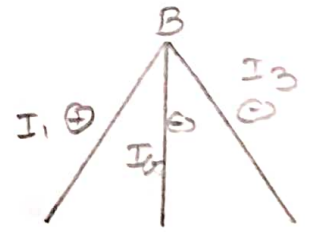- Current Rule (or) Junction Rule
- Voltage Rule (or) Loop Rule
- PQRS → Resistance
- I_1, I_2, I_3, I_4 → current
- ABCD → Junction
- \mathcal{E} → emf
- I_G → galvanometer meter
- emf → electro motive force



B Junction } current law
 D Junction }
 B Junction (current law) Rule
 $I_1 - I_2 - I_3 = 0 \rightarrow 0$

D Junction (Current Rule)

$$I_2 + I_G - I_4 = 0 \rightarrow (1)$$

ABDA (Voltage Rule)

Junction

$$I_{1P} + I_{GQ} - I_{3R} = 0 \rightarrow (2)$$

ABCD Junction

$$I_{1P} + I_{3Q} - I_{4S} - I_{2R} = 0 \rightarrow (3)$$

no current galvanometer null deflection

$$I_G = 0$$

From equation (1)

$$I_1 - I_G - I_3 = 0$$

$$I_1 - 0 - I_3 = 0$$

$$I_1 - I_3 = 0$$

$$\boxed{I_1 = I_3} \rightarrow (4)$$

From equation (2)

$$I_2 + I_G - I_4 = 0$$

$$I_2 + 0 - I_4 = 0$$

$$I_2 - I_4 = 0$$

$$\boxed{I_2 = I_4} \rightarrow (5)$$


From equation (3)

$$I_{1P} + I_{GQ} - I_{2R} = 0$$

$$I_{1P} + 0 - I_{2R} = 0$$

$$I_{1P} - I_{2R} = 0$$
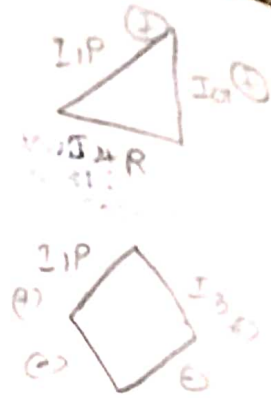
$$\boxed{I_{1P} = I_{2R}} \rightarrow (6)$$



From equation (4)

$$I_1 P + I_2 Q - I_4 S - I_2 R = 0$$

$$I_1 P - I_2 S - I_2 R = 0$$

$$I_1 P = I_2 (S + R) = 0$$

$$I_1 (P + Q) = I_2 (S + R) \rightarrow (8)$$

$$I_1 = I_2 \rightarrow (5)$$

$$I_2 = I_4 \rightarrow (6)$$

$$I_1 P = I_2 R \rightarrow (7)$$

(8)/(7)

$$\frac{I_1 (P + Q)}{I_1 P} = \frac{I_2 (S + R)}{I_2 R}$$

$$\frac{P + Q}{P} = \frac{R + S}{R}$$

$$1 + \frac{Q}{P} = 1 + \frac{S}{R}$$

$$\frac{Q}{P} = \frac{S}{R}$$

$$\frac{P}{Q} = \frac{R}{S} \rightarrow (9)$$

Dr. G. THIRUMOORTHY, M.Sc., B.Ed., Ph.D.,
Guest Lecture
PG and Research Department of Physics
Government Arts College (Autonomous)
SALEM - 636 007.

8610560810

Pg: 107

2 mark

Example 2.23

In a wheatstone's bridge $P = 100 \Omega$, $Q = 1000 \Omega$ and $R = 40 \Omega$. If the galvanometer shows zero deflection determine the value of S

Solution:

$$P = 100 \Omega$$

$$Q = 1000 \Omega$$

$$R = 40 \Omega$$

$$S = ?$$

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{P}{Q} = R \left(\frac{1}{S} \right)$$

$$\frac{P}{RQ} = \frac{1}{S}$$

$$S = \frac{R\theta}{P}$$

$$S = \frac{40 \times 1000}{100}$$

$$S = 40 \times 10$$

$$S = 400 \Omega$$

Dr. G. THIRUNADORTHY, M.Sc., B.Ed., Ph.D.,
(Guest Lecturer)
P.G. and Research Department of Physics
Government Arts College (Autonomous)
SALEM - 636 007.

86 10 56 08 10