

UNIT-2

CURRENT ELECTRICITY

Current Electricity

Charge \rightarrow Moving \rightarrow current (I)

$$I = Q/t$$

unit: Ampere (A)

I \rightarrow current

Q \rightarrow charge

t \rightarrow taken time

Pg: 82

Solution

①

$$\text{charge } (Q) = 120 \text{ C}$$

copper wire (Cu)

time = 1 minutes

current $I = ?$

$$I = \frac{Q}{t}$$

$$I = \frac{120}{1 \times 60} = \frac{120}{60} = \frac{12}{6} = 2 \text{ A}$$

②

$$\text{charge } (Q) = 120 \text{ C}$$

copper wire (Cu)

time = 1 second

current $I = ?$

$$I = \frac{Q}{t}$$

$$I = \frac{120}{1}$$

$$I = 120 \text{ A}$$

(Creative Question)

Pg: 86

3 mark

⑦ ⑧ ⑨

Example : 2.4

determine the number of electrons flowing per second through a conductor when a current of 32 A flows through it

Solution:

$$I = 32 \text{ A}$$

$$t = 1 \text{ second}$$

$$n = ?$$

$n \rightarrow$ number of electron = ?

$$I = \frac{Q}{t} \quad Q = nq$$

$$I = \frac{q}{t} \quad q = ne$$

$$I = \frac{nq}{t}$$

$$I \times t = nq$$

$$n = \frac{It}{e}$$

$$e = 1.6 \times 10^{-19} \text{ C}$$

$$n = \frac{32 \times 1}{1.6 \times 10^{-19}}$$

$$n = \frac{32}{1.6} \times 10^{19}$$

$$n = 20 \times 10^{19}$$

$$n = 2 \times 10^1 \times 10^{19}$$

$$n = 2 \times 10^{20} \text{ electron}$$

ohm's law

$$I \propto V$$

$$V = IR$$

Current increases

Potential difference increases

V → potential difference → unit → Volt (V)

I → current → unit → Ampere (A)

R → Resistance → unit → ohm (Ω)

$$R \propto I \downarrow$$

$$R \downarrow I \propto$$



Battery






Resistance



variable Resistance



capacitor

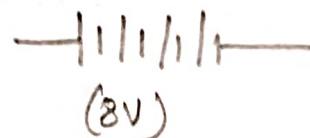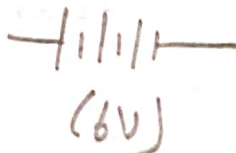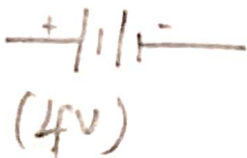


pg: 88
2 mark

Example: 2.5

A potential difference across 24Ω resistor is $12V$. What is the current through the resistor?

Solution:

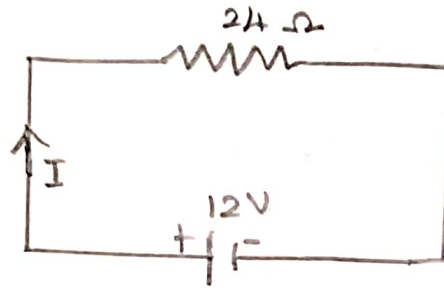

Resistance $R = 24 \Omega$

potential difference $V = 12V$

current $I = ?$

Applying Ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{12}{24}$$

$$I = \frac{12}{2 \times 12}$$


$$I = \frac{1}{2}$$

$$I = 0.5A$$

Dr. G. THIRU... RTHI, M.Sc., B.Ed., Ph.D.,
Guest Lecture
PG and Research Department of Physics
Government Arts College (Autonomous)
S. E. N. 107.

pg: 90
3 mark

Resistance series connection

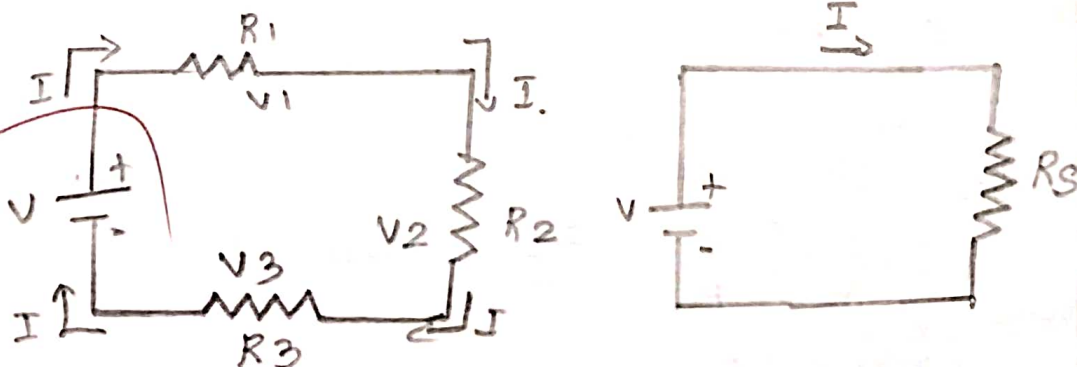

Applying ohm's law

$$V = IR$$

$$V_1 = IR_1 \rightarrow \textcircled{1}$$

$$V_2 = IR_2 \rightarrow \textcircled{2}$$

$$V_3 = IR_3 \rightarrow \textcircled{3}$$

Total potential difference

$$V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3$$


$$V = I(R_1 + R_2 + R_3)$$

$$V = IR_S$$

$$IR_S = I(R_1 + R_2 + R_3)$$

$$R_S = R_1 + R_2 + R_3$$

Example 2.8

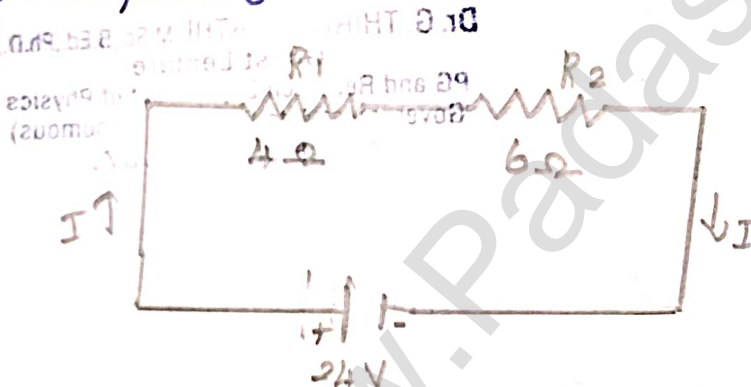

- i) R_S ii) I iii) V_1 iv) V_2

$$i) R_S = R_1 + R_2$$

$$R_S = 4 + 6$$

$$= 10 \Omega$$

$$ii) V = IR$$

$$I = \frac{V}{R} = \frac{V}{R_S} = \frac{24}{10} = 2.4 \text{ A}$$

$$iii) V_1 = IR_1$$

$$V_1 = 2.4 \times 4$$

$$V_1 = 9.6 \text{ V}$$



$$IV) V_2 = IR_2$$

$$V_2 = 2.4 \times 6$$

$$V_2 = 14.4$$

pg: 91

Resistors in parallel connection

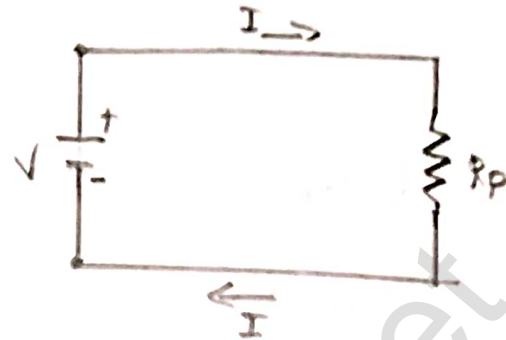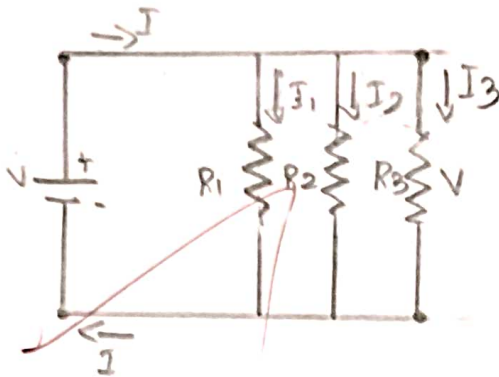

$$I = I_1 + I_2 + I_3$$

Applying Ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_1 = \frac{V}{R_1} \rightarrow \textcircled{1}$$

$$I_2 = \frac{V}{R_2} \rightarrow \textcircled{2}$$

$$I_3 = \frac{V}{R_3} \rightarrow \textcircled{3}$$

Total current

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I = \frac{V}{R_p}$$

$$\frac{V}{R_p} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Dr. G. THIRUMONTHI, M.Sc., B.Ed., P.D.
 Guest Lecture
 PG and Research Department of Physics
 Government Arts College (Autonomous)
 SALEM - 636 007.
 8610560810.

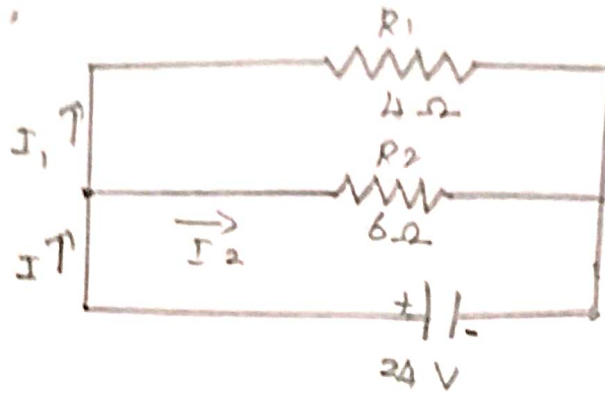Example 2.9Solution

i) $1/R_p = ?$ ii) $I_1 = ?$ iii) $I_2 = ?$ iv) $I = ?$

i) $1/R_p$

$$1/R_p = 1/R_1 + 1/R_2$$

$$1/R_p = 1/4 + 1/6$$

$$1/R_p = \left(\frac{1 \times 3}{4 \times 3} \right) + \left(\frac{1 \times 2}{6 \times 2} \right)$$

$$1/R_p = \frac{3}{12} + \frac{2}{12} = \frac{3+2}{12}$$

$$1/R_p = \frac{5}{12}$$

$$R_p = \frac{12}{5} \Omega$$

ii) $I_1 = ?$

Applying Ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_1 = \frac{V}{R_1}$$

$$I_1 = \frac{24}{4}$$

$$I_1 = 6 \text{ A}$$

iii) $I_2 = ?$

Applying Ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_2 = \frac{V}{R_2}$$

$$I_2 = \frac{24}{6}$$

$$I_2 = 4A$$


∴ I = ?

$$I = I_1 + I_2$$

$$I = 6 + 4$$

$$I = 10A$$

Example : 2.11

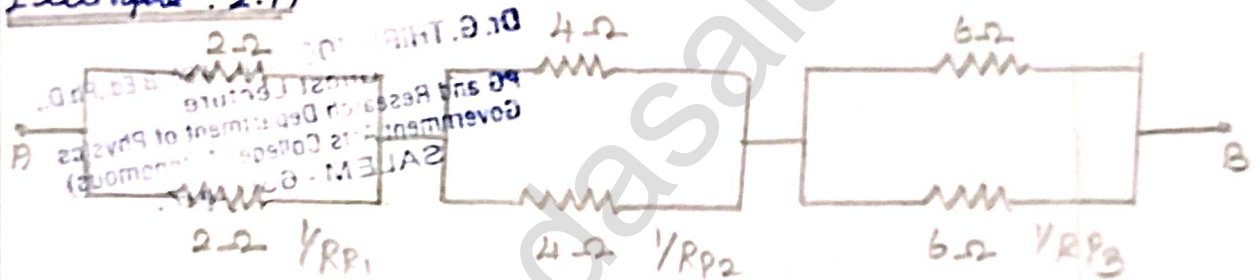

Solution : 1st - diagram

$$i) \frac{1}{R_{p1}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{p1}} = \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{R_{p1}} = \frac{1+1}{2}$$

$$\frac{1}{R_{p1}} = \frac{2}{2} = 1$$

$$R_{p1} = 1\Omega$$

2nd → diagram

$$ii) \frac{1}{R_{p2}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{P2}} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R_{P2}} = \frac{1+1}{4}$$

$$\frac{1}{R_{P2}} = \frac{2}{4}$$

$$R_{P2} = 4/2$$

$$R_{P2} = 2 \Omega$$

iii) 3rd → Diagram

$$\frac{1}{R_{P3}} = \frac{1}{6} + \frac{1}{6}$$

$$\frac{1}{R_{P3}} = \frac{1+1}{6}$$

$$\frac{1}{R_{P3}} = \frac{2}{6}$$

$$\frac{1}{R_{P3}} = \frac{2}{6}$$

$$R_{P3} = 6/2$$

$$R_{P3} = 3 \Omega$$

$$R_S = R_{P1} + R_{P2} + R_{P3}$$

$$R_S = 1 + 2 + 3$$

$$R = 6 \Omega$$

Dr. G. THIRUMORTHY, M.Sc., B.Ed., Ph.D.,
Guest Lecture
PG and Research Department of Physics
Government Arts College (Autonomous)
SALEM - 636 007.

8610560810