I ANSWER THE FOLLOWING QUESTIONS	
	10X 2=20
1. Why current is a scalar?	
2. Define temperature coefficient of resistance	
3. What is electric power and electric energy?	
4. State Kirchhoff's rule.	N
5. State Joule's law of heating	
6. What is meant by Fraunhofer lines?	
7. Write down the integral form of modified Amper	e's circuital law
8 What is displacement current	
9. Explain the concept of intensity of electromagne	etic waves
10. Define current density.	
II ANSWER THE FOLLOWING QUESTIONS	7 X 3=21
1. Explain the determination of the internal resista voltmeter.	nce of a cell using
2. How the emf of two cells are compared using po	tentiometer?
3. Explain the equivalent resistance of a parallel re	esistor network
4. A copper wire of 10-6 m2 area of cross section, ca	arries a current of 2
A. If the number of electrons per cubic meter is 8 > current density and average drift velocity.	< 10 ²⁸ , calculate the
5. A transmitter consists of LC circuit with an induc	stance of 1 μ H and a
capacitance of 1 μ F. What is the wavelength of the e waves it emits?	electromagnetic
6.Two cells each of 5V are connected in series acros	ss a 8 Ω resistor and
three parallel resistors of 4 Ω , 6 Ω and 12 Ω . Draw a c	ircuit diagram for
the above arrangement. Calculate i) the current dr	awn from the cell
(ii) current through each resisistor	
7. A magnetron in a microwave oven emits electror	
waves) with frequency f = 2450 MHz. What magneti	-
required for electrons to move in circular paths wit	in this irequency?.

MODEL QUESTION PAPER	MARKS 70
I ANSWER THE QUESTION QUESTION	4 X 5=20
. Obtain the condition for bridge balance	e in Wheatstone's bridge.
. Measurement ofinternal resistance of a	cell by potentiometer
. What is emission spectra?. Give their ty	pes.
. Write down Maxwell equations in integ	ral form
.NAGARAJAN (PHYSICS TEACHER)	
IOUNT CAREML MATRIC HR SEC SCHOOL	

Kindly Send me Your Key Answer to Our email id - Padasalai.net@gmail.Com