

SIR CV RAMAN COACHING CENTRE –IDAPPADI,SALEM ,

XLL PHYSICS UNIT – 2 -2025

Date ; 01.01.2025

Lesson – 2

VERY VERY IMPORTANT QUESTIONS

English medium

JUST PASS MATERIAL

PREPARED BY

Dr.G.THIRUMOORTHY, M.Sc, B.Ed, Ph..D , PHYSICS ,,,


8610560810, 8883610465,,,

thiruphysics1994@gmail.com

QUESTIONS :

- 1. Microscopic model of current (or) Describe the microscopic model of current and obtain microscopic form of Ohm's law**
- 2. OHM'S LAW (or) Obtain the macroscopic form of Ohm's law from its microscopic form and discuss its limitation**
- 3. Resistors in series and parallel (or) Explain the equivalent resistance of a series and parallel resistor network**
- 4. Resistors in series and parallel (or) Explain the equivalent resistance of a series and parallel resistor network**
- 5. Determination of internal resistance (or) Explain the determination of the internal resistance of a cell using voltmeter**
- 6. Cells in series**
- 7. Cells in parallel**
- 8. Wheatstone's bridge (or) Obtain the condition for bridge balance in Wheatstone's bridge**
- 9. Meter bridge (or) Explain the determination of unknown resistance using meter bridge**
- 10. Comparison of emf of two cells with a potentiometer (or) How the emf of two cells are compared using potentiometer**

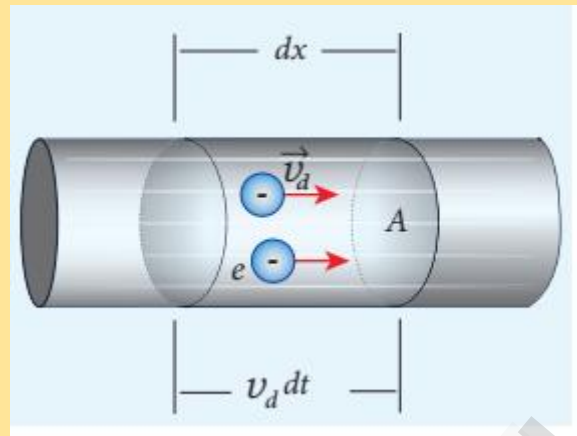1. **Microscopic model of current (or)** Describe the microscopic model of current and obtain microscopic form of Ohm's law



$$v_d = \frac{dx}{dt}; \quad dx = v_d dt$$



$$J = nev_d$$

$$I = neAv_d$$

$$\vec{j} = -\sigma \vec{E}$$

$$\rho = \frac{1}{\sigma} = \frac{m}{ne^2\tau}$$

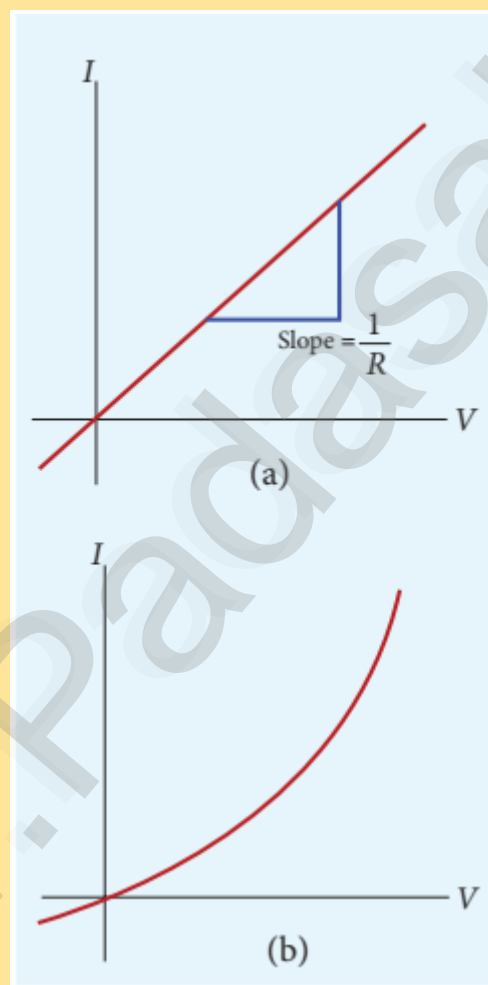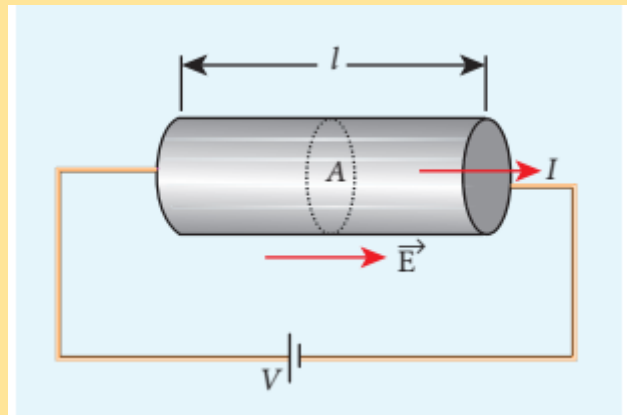2. **OHM'S LAW** (or) Obtain the macroscopic form of Ohm's law from its microscopic form and discuss its limitation




$$J = \sigma E = \sigma \frac{V}{l}$$

$$V = I \left(\frac{l}{\sigma A} \right)$$

$$V = IR$$

$$R = \frac{V}{I}$$

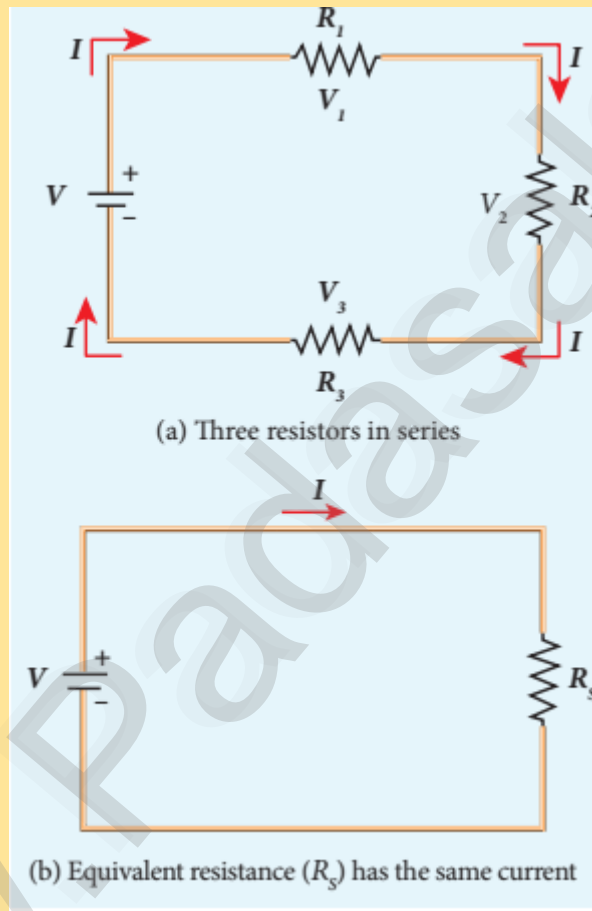3. **Resistors in series and parallel (or)** Explain the equivalent resistance of a series and parallel resistor network.



$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3$$


$$V = I(R_1 + R_2 + R_3)$$

$$V = IR_c$$

$$R_s = R_1 + R_2 + R_3$$

The value of equivalent resistance in series connection will be greater than each individual resistance

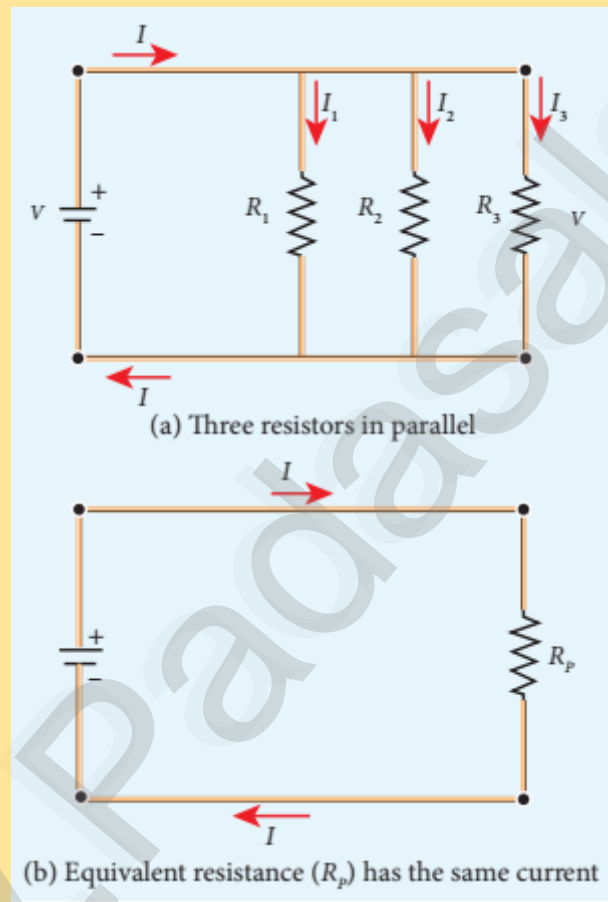4. Resistors in parallel (or) Explain the equivalent resistance of a series and parallel resistor network.



$$I = I_1 + I_2 + I_3$$

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3}$$


$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$I = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

The value of equivalent resistance in parallel connection will be lesser than each individual resistance.

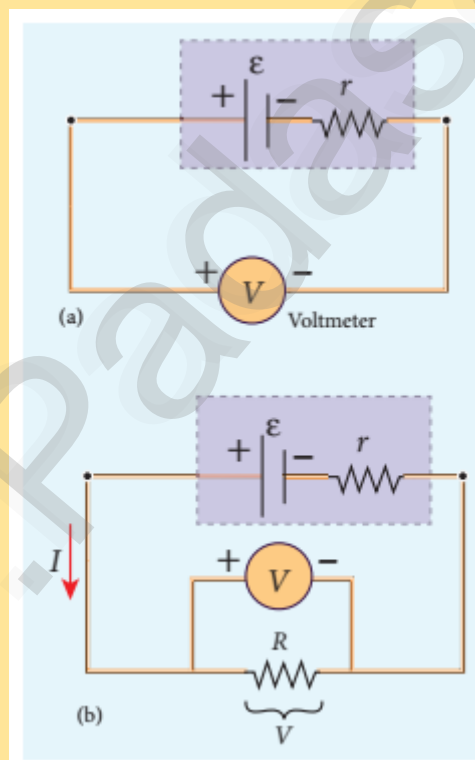5. Determination of internal resistance (or) Explain the determination of the internal resistance of a cell using voltmeter




$$V = IR$$

$$Ir = \epsilon - V$$

$$r = \left[\frac{\epsilon - V}{V} \right] R$$

$$P = I^2 R + I^2 r$$

6. Cells in series

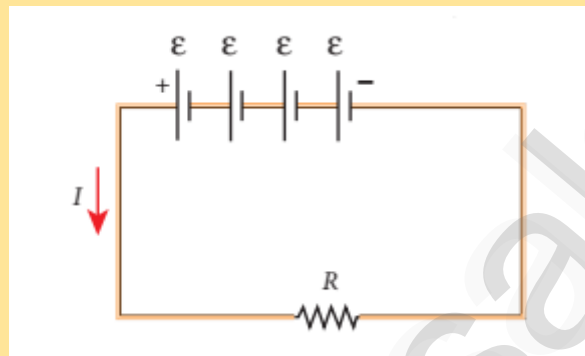


$$I \approx \frac{n\epsilon}{R} \approx nI_1$$

$$I = \frac{\text{total emf}}{\text{total resistance}} = \frac{n\epsilon}{nr + R}$$

$$\left(I_1 = \frac{\epsilon}{R} \right)$$

$$\text{Case (b) If } r \gg R, I = \frac{n\epsilon}{nr} \approx \frac{\epsilon}{r}$$

7.Cells in parallel

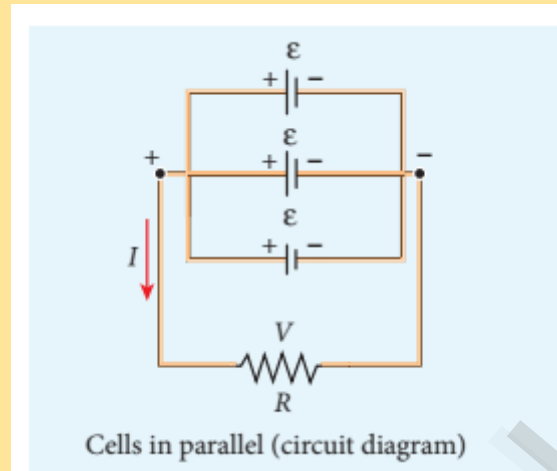

Cells in parallel (circuit diagram)


$$I = \frac{\epsilon}{\frac{r}{n} + R}$$

$$I = \frac{n\epsilon}{r + nR}$$

Case (a) If $r \gg R$, $I = \frac{n\epsilon}{r} = nI_1$

Case (b) If $r \ll R$, $I = \frac{\epsilon}{R}$

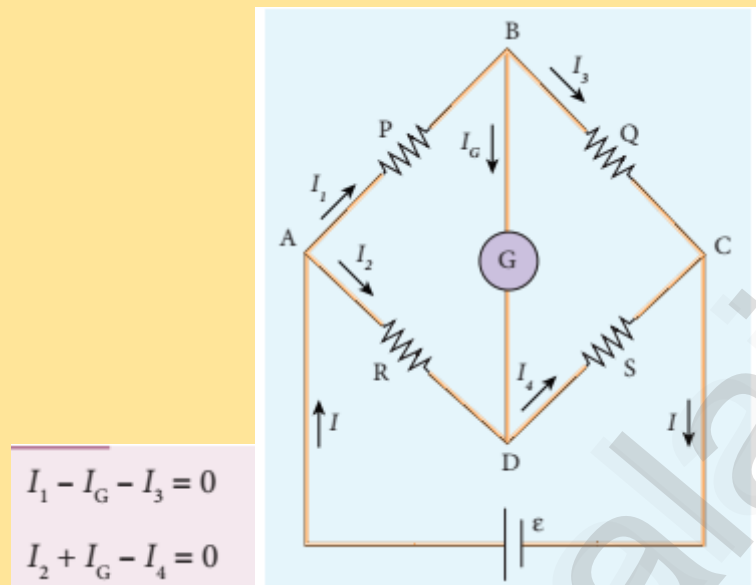8. **Wheatstone's bridge (or)** Obtain the condition for bridge balance in Wheatstone's bridge



$$I_1 - I_G - I_3 = 0$$

$$I_2 + I_G - I_4 = 0$$

$$I_1 P + I_G G - I_2 R = 0$$

$$I_1 P + I_3 Q - I_4 S - I_2 R = 0$$

$$I_1 = I_3$$


$$I_2 = I_4$$

$$I_1 P = I_2 R$$

$$I_3 Q = I_4 S$$

$$\frac{P}{Q} = \frac{R}{S}$$

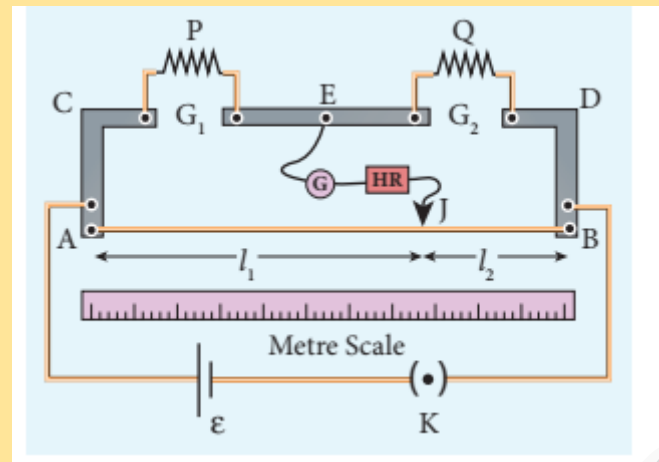9. Meter bridge (or) Explain the determination of unknown resistance using meter bridge.



$$\frac{P}{Q} = \frac{R}{S} = \frac{r \cdot AJ}{r \cdot JB}$$


$$\frac{P}{Q} = \frac{AJ}{JB} = \frac{l_1}{l_2}$$

$$\text{Resistance} = \rho \frac{l}{A}$$

$$P = Q \frac{l_1}{l_2}$$

$$\rho = P \frac{\pi a^2}{l}$$

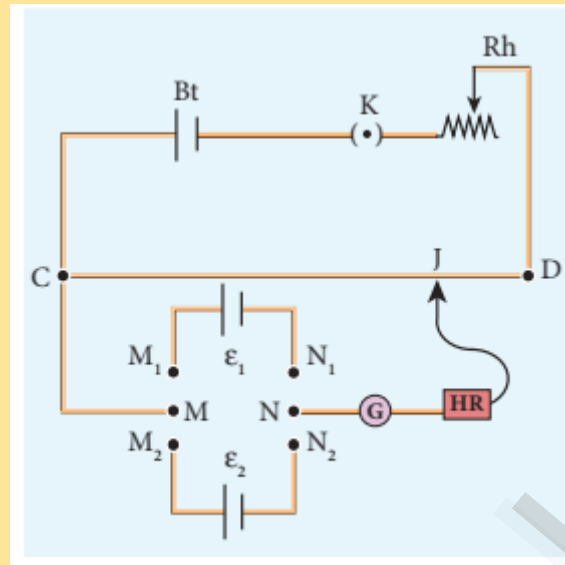10. Comparison of emf of two cells with a potentiometer (or) How the emf of two cells are compared using potentiometer?



we have $\epsilon_1 = Irl_1$

$\epsilon_2 = Irl_2$

$$\frac{\epsilon_1}{\epsilon_2} = \frac{l_1}{l_2}$$

PREPARED BY

Dr.G.THIRUMOORTHY,M.Sc,B.Ed,Ph..D ,PHYSICS

8610560810,8883610465,,,

thiruphysics1994@gmail.com

www.Padasalai.Net