
12 th PHYSICS

UNIT 1 & 2

IMPORTANT FORMULAE

Padasalai

**MR. THIVIYARAJ V,
M.Sc.,M.Phill.,B.Ed**

UNIT 1 - ELECTROSTATICS

1. Coulomb's law, $\vec{F}_{21} = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2} \hat{r}_{12}$

2. Electric field due to a point charges ,

$$\vec{E} = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} \hat{r}$$

3. Electric dipole moment , $\vec{P} = 2q\vec{d}$

4. Electric field due to a dipole along its axial line ,

$$\vec{E}_{\text{tot}} = \frac{1}{4\pi\epsilon_0} \cdot \frac{2\vec{P}}{r^3}$$

5. Electric field due to a dipole along its equatorial line ,

$$\vec{E}_{\text{tot}} = \frac{1}{4\pi\epsilon_0} \frac{\vec{P}}{r^3}$$

6. Torque experience by an electric dipole in a uniform electric field .

$$\vec{\tau} = \vec{P} \times \vec{E} ; \tau = qE2a \sin \theta$$

7. Electric potential at a point due to a point charge,

$$V = \frac{1}{4\pi\epsilon_0} \frac{q}{r}$$

8. Electric potential at a point due to electric field ,

$$V = \frac{1}{4\pi\epsilon_0} \frac{P}{r^2} \cos \theta = \frac{1}{4\pi\epsilon_0} \frac{\vec{P} \cdot \vec{r}}{r^2}$$

9. Electric field $E = -\frac{dv}{dx} = -\left[\frac{\partial v}{\partial x} \hat{i} + \frac{\partial v}{\partial y} \hat{j} + \frac{\partial v}{\partial z} \hat{k}\right]$

10. Electrostatic potential energy between two charges is ,

$$U = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r}$$

11. Electrostatic potential energy between three charges is ,

$$U = \frac{1}{4\pi\epsilon_0} \left[\frac{q_1 q_2}{r_{12}} + \frac{q_1 q_3}{r_{13}} + \frac{q_2 q_3}{r_{23}} \right]$$

12. Electrostatic potential energy stored in a dipole in an uniform electric field ,

$$U = -PE\cos\theta = -\vec{P} \cdot \vec{E}$$

13. Electrostatic potential energy difference between two angular positions θ and θ^l of a dipole kept in an uniform electric field ,

$$\Delta U = -PE\cos\theta + PE\cos\theta^l$$

14. Electric flux , $\Phi_E = \vec{E} \cdot \vec{A} = EA\cos\theta$

15. Total electric flux through a closed surface ,

$$\Phi_E = \frac{Q_{net}}{\epsilon_0}$$

16. Electric field due to an infinitely long charged wire is,

$$E = \frac{\lambda}{2\pi r\epsilon_0}$$

17. Electric field due to charged infinite plane sheet is,

$$E = \frac{\sigma}{2\epsilon_0}$$

18. Electric field due to two parallel charged infinite sheet at a point between the sheet

$$E = \frac{\sigma}{\epsilon_0}$$

19. Electric field due to uniformly charged spherical shell of radius 'R' at a point outside the shell ,

$$E = \frac{1}{4\pi\epsilon_0} \frac{Q}{r^2}$$

20. Electric field due to uniformly charged spherical shell of radius 'R' at a point on the shell ,

$$E = \frac{1}{4\pi\epsilon_0} \frac{Q}{R^2}$$

21. For a parallel plate capacitor,

$$\text{Electric field , } E = \frac{Q}{\epsilon_0 A}$$

$$\text{Potential difference , } V = \frac{Q \cdot d}{\epsilon_0 A}$$

$$\text{Capacitance , } C = \frac{\epsilon A}{d}$$

22. (a) Battery is disconnected from the capacitor and a dielectric is inserted between the plates ,

$$C_0 = \frac{Q_0}{V_0} , \quad E = \frac{E_0}{\epsilon_r} , \quad V = \frac{V_0}{\epsilon_r} , \quad C = \frac{\epsilon_r \epsilon_0 A}{d} , \quad U_0 = \frac{1}{2} C_0 V_0^2 , \quad U = \frac{U_0}{\epsilon_r}$$

- (b) Battery remains connected and a dielectric inserted between the plates of the capacitor ,

$$Q = \epsilon_r Q_0 , \quad C = \epsilon_r C_0 , \quad C = \frac{\epsilon_r \epsilon_0 A}{d} , \quad U_0 = \frac{1}{2} C_0 V_0^2 , \quad U = \epsilon_r U_0$$

23. Capacitor in series : $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

$$\text{Capacitor in parallel : } C_P = C_1 + C_2 + C_3$$

24. Two charged spheres connected through a wire ,

$$\frac{q_1}{r_1} = \frac{q_2}{r_2} , \quad Q = q_1 + q_2 , \quad \sigma_1 r_1 = \sigma_2 r_2 .$$

$$q_2 = Q \left[\frac{r_2}{r_1 + r_2} \right]$$

25. In van de graaff generator , maximum potential difference created ,

$$V_{max} = 10^7 \text{ V.}$$

UNIT 2- CURRENT ELECTRICITY

1. ELECTRIC CURRENT [I] => Ampere

$$I = \frac{Q}{t}$$

Q => Charge ; t => time.

2. INSTANTANEOUS CURRENT [I]

$$I = \frac{dQ}{dt}$$

3. DRIFT VELOCITY [\vec{V}_d] => ms⁻¹

$$V_d = a\tau$$

$$V_d = -\frac{e\tau}{m}E$$

$$V_d = -\mu E$$

μ => Mobility of the electron

a => Accceleration

τ => Mean time

E => Electric field

m => mass of the electron

e => 1.6×10^{-19} C

4. RELATION BETWEEN CURRENT AND DRIFT VELOCITY

$$I = nAeV_d$$

n => Electrons per unit volume

A => Area of cross section

5. CURRRENT DENSITY [J] => Am⁻²

$$J = \frac{I}{A}$$

$$J = neV_d$$

$$J = + \sigma E$$

σ => Conductivity [$\Omega^{-1} \text{ m}^{-1}$]

$$\sigma = \frac{n.e^2\tau}{m}$$

6. RESISTANCE [R] =>ohm [Ω]

$$R = \frac{V}{I}$$

$$R = \frac{\rho l}{A}$$

V => Potential difference

$$V = I R$$

7. RESISTIVITY [ρ] => ohm m [Ωm]

$$\rho = \frac{RA}{l}$$

$$\rho = \frac{1}{\sigma} = \frac{m}{n.e^2\tau}$$

8. RESISTORS IN SERIES [R_s]

$$R_s = R_1 + R_2 + R_3$$

No of resistors connected in series ,

$$R_s = nS$$

9. RESISTORS IN PARALLEL [R_p]

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

No of resistors connected in parallel ,

$$R_p = \frac{R}{n}$$

10. TEMPERATURE COEFFICIENT OF RESISTIVITY [α] => / $^{\circ}C$

$$\alpha = \frac{\Delta\rho}{\rho_0\Delta T} = \frac{\rho_T - \rho_0}{\rho_0[T - T_0]} \quad [T_0 = 20^{\circ}C]$$

11. RESISTANCE OF A CONDUCTOR AT TEMPERATURE => $T^{\circ}C$

$$R_T = R_0 [1 + \alpha [T - T_0]]$$

$$\alpha = \frac{R_T - R_0}{\rho_0 [T - T_0]}$$

 R_T => Resistance of a conductor at $T^{\circ}C$ R_0 => Resistance of a conductor at some [$20^{\circ}C$] reference temperature

12. ELECTRIC POWER [P] => watt

$$P = V I$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

13. ELECTRIC ENERGY => Watt hour

$$\text{Energy} = VIT$$

$$1 \text{ Kwh} = 1000 \text{ wh} = 3.6 \times 10^6 \text{ J}$$

1 Kwh= 1 unit of electrical energy

14. INTERNAL RESISTANCE OF A CELL [r] => Ohm (Ω)

$$r = \left[\frac{\xi - V}{V} \right] R$$

ξ = > EMF of the cell

15. CELLS IN SERIES

$$I = \frac{n \xi}{nr + R}$$

a) [$r \gg R$] => $I \approx \frac{\xi}{r}$ [Advantages]

b) [$r \ll R$] => $I \approx nI_1$

16. CELLS IN PARALLEL

$$I = \frac{n \xi}{r + nR}$$

a) [$r \gg R$] => $I = nI_1$ [Advantages]

b) [$r \ll R$] => $I = \frac{\xi}{r}$

17. BRIDGE BALANCE CONDITION [WHEATSTONE'S BRIDGE]

$$\frac{P}{Q} = \frac{R}{S}$$

P , Q ,R and S are resistors

18. METER BRIDGE

The value of unknown resistance

$$P = Q \frac{l_1}{l_2}$$

$l_1, l_2 \Rightarrow$ Balancing length

Resistivity of the material

$$\rho = P \frac{\pi r^2}{l}$$

$a \Rightarrow$ Radius of the wire

$l \Rightarrow$ length of the wire

19. POTENTIOMETER

EMF of the cell

$$\xi = Irl$$

Comparison of the two cells

$$\frac{\xi_1}{\xi_2} = \frac{l_1}{l_2}; \xi_1 = \xi_2 \frac{l_1}{l_2}; \xi_2 = \xi_1 \frac{l_2}{l_1}$$

Internal resistance

$$r = R \left[\frac{l_1 - l_2}{l_2} \right]$$

20. JOULE 'S LAW [HEAT]

$$H = VIt$$

$$H = I^2 R t$$

21. ONE AMPERE

$$1A = \frac{1C}{1s}$$

22. ONE OHM

$$1\Omega = \frac{1V}{1A}$$


PG.NO:

MR.THIVİYARAJ V.,M.Sc.,M.Phill.,M.Ed

1

CURRENT ELECTRICITY**UNSOLVED PROBLEMS**

1. The following graphs represent the current versus voltage and voltage versus current for the six conductors A, B, C, D, E and F. Which conductor has least resistance and which has maximum resistance?

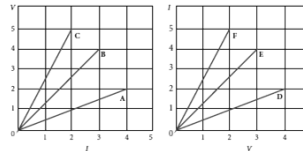Solution

According to ohm's law,

$$V = IR; R = \frac{V}{I}$$

GRAPH 1:

A : slope = $R_A = \frac{\Delta V}{\Delta I} = \frac{2}{4} = 0.5 \Omega$

B : slope = $R_B = \frac{\Delta V}{\Delta I} = \frac{4}{3} = 1.33 \Omega$

C : slope = $R_C = \frac{\Delta V}{\Delta I} = \frac{5}{2} = 2.5 \Omega$

GRAPH 2:

D : slope = $R_D = \frac{\Delta V}{\Delta I} = \frac{4}{2} = 2 \Omega$

E : $\frac{1}{\text{slope}} = R_E = \frac{\Delta V}{\Delta I} = \frac{3}{4} = 0.75 \Omega$

F : $\frac{1}{\text{slope}} = R_F = \frac{\Delta V}{\Delta I} = \frac{2}{5} = 0.4 \Omega$

Least Resistance, $R_F = 0.4 \Omega$

Maximum Resistance, $R_C = 2.5 \Omega$

PG.NO:

MR.THIVYARAJ V.,M.Sc.,M.Phill.,M.Ed

2

2. Lightning is very good example of natural current. In typical lightning, there is 10^9 J energy transfer across the potential difference of 5×10^7 V during a time interval of 0.2 s.

Solution

$$W = 10^9 \text{ J}; V = 5 \times 10^7 \text{ V}; t = 0.2 \text{ s} = 2 \times 10^{-1} \text{ s}.$$

1. Total amount of charge:

$$W = V \cdot q$$

$$q = \frac{W}{V} = \frac{10^9}{5 \times 10^7} = 0.2 \times 10^2$$

$$\boxed{q = 20 \text{ C}}$$

2. CURRENT : $I = Q/t$

$$= \frac{20}{2 \times 10^{-1}} = 100 \text{ A}$$

3. POWER : $P = VI$

$$= 5 \times 10^7 \times 10^2 = 5 \times 10^9 \text{ W}$$

$$\boxed{P = 5 \text{ GW}}$$

3. A copper wire of 10^{-6} m^2 area of cross section, carries a current of 2 A. If the number of free electrons per cubic meter in the wire is 8×10^{28} , calculate the current density and average drift velocity of electrons.

Solution

SOLUTION:

$$J = I/A = 2/10^{-6} = 2 \times 10^6 \text{ A m}^{-2}$$

$$J = neV_d$$

$$V_d = \frac{J}{ne} = \frac{2 \times 10^6}{8 \times 10^{28} \times 1.6 \times 10^{-19}}$$

$$= \frac{10^{-3}}{6.4} = 1.56 \times 10^{-4} \text{ m/s}$$

$$\boxed{V_d = 15.6 \times 10^{-5} \text{ m s}^{-1}}$$

PG.NO:

MR.THIVYARAJ V.,M.Sc.,M.Phill.,M.Ed

3

4. The resistance of a nichrome wire at 20°C is $10\ \Omega$. If its temperature coefficient of resistivity of nichrome is $0.004/^{\circ}\text{C}$, find the resistance of the wire at boiling point of water. Comment on the result.

Solution

$$\alpha = \frac{R_T - R_0}{R_0 [T - T_0]}$$

$$\begin{aligned} 0.004 &= \frac{R_{100} - 10}{10 [100 - 20]} \\ &= \frac{R_{100} - 10}{10 [80]} \end{aligned}$$

$$[0.004 \times 800] = R_{100} - 10$$

$$3.2 + 10 = R_{100}$$

$$\boxed{R_{100} = 13.2\ \Omega}$$

[OR]

$$R_t = R_0 [1 + \alpha (T - T_0)]$$

$$R_{100} = 10 [1 + 0.004 [100 - 20]]$$

$$R_{100} = 10 [1 + 0.32] = 13.2\ \Omega$$

5. The rod given in the figure is made up of two different materials.



Both have square cross sections of 3 mm side. The resistivity of the first material is $4 \times 10^{-3}\ \Omega\text{m}$ and that of second material has resistivity of $5 \times 10^{-3}\ \Omega\text{m}$. What is the resistance of rod between its ends?

PG.NO:

4

MR.THIVIYARAJ V.,M.Sc.,M.Phill.,M.Ed

Solution

$$P_1 = 4 \times 10^{-3} \text{ m} ; l_1 = 25 \text{ cm} .$$

$$P_2 = 5 \times 10^{-3} \text{ m} ; l_2 = 70 \text{ cm} .$$

$$\text{side length} = 3 \text{ mm} .$$

$$\text{Area } A = [3 \times 10^{-3} \text{ m}]^2$$

$$A = 9 \times 10^{-6} \text{ m}^2 .$$

SOLUTION:

$$R_S = R_1 + R_2$$

$$R_1 = \frac{P_1 l_1}{A} = \frac{4 \times 10^{-3} \times 25 \times 10^{-2}}{9 \times 10^{-6}}$$

$$= \frac{4 \times 25 \times 10^{-5}}{9 \times 10^{-6}} = \frac{1000}{9} \Omega$$


$$R_2 = \frac{P_2 l_2}{A} = \frac{5 \times 10^{-3} \times 70 \times 10^{-2}}{9 \times 10^{-6}}$$

$$= \frac{5 \times 70 \times 10^{-5}}{9 \times 10^{-6}} = \frac{3500}{9} \Omega$$

$$R_S = \frac{1000}{9} + \frac{3500}{9} = \frac{4500}{9}$$

$$R_S = 500 \Omega$$

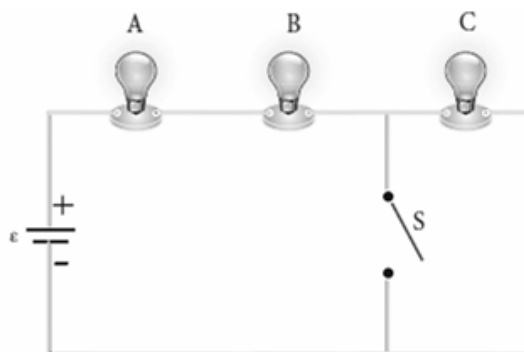6. Three identical lamps each having a resistance R are connected to the battery of emf ε as shown in the figure.



PG.NO:

MR.THIVIYARAJ V.,M.Sc.,M.Phill.,M.Ed

5

Suddenly the switch S is closed. (a) Calculate the current in the circuit when S is open and closed (b) What happens to the intensities of the bulbs A,B and C. (c) Calculate the voltage across the three bulbs when S is open and closed (d) Calculate the power delivered to the circuit when S is opened and closed (e) Does the power delivered to the circuit decrease, increase or remain same?

Solution

a) CURRENT:

ohm's law $\frac{V}{R} = I$ $V = IR$
 $\mathcal{E} = V.$

$$R_1 = R_2 = R_3 = R$$

Three lamps are connected in series, $R_s = R_1 + R_2 + R_3.$

$$R_s = R + R + R = 3R.$$

Switch is open:

$$I = \frac{V}{R_s} = \frac{\mathcal{E}}{3R}.$$

Switch is closed:

No current flow through lamp 'c'.

$$I = \frac{\mathcal{E}}{2R}.$$

b) INTENSITIES:Switch is open:

All bulbs having equal intensities.

Switch is closed:

A and B equal intensities
But 'C' will not glow.
because no current.

c) VOLTAGE:Switch is open:

$$I = \mathcal{E}/3R$$

$$V_A = IR = \mathcal{E}/3R \times R = \mathcal{E}/3$$

$$V_B = IR = \mathcal{E}/3R \times R = \mathcal{E}/3$$

$$V_C = IR = \mathcal{E}/3R \times R = \mathcal{E}/3$$

Switch is closed:

$$V_A = IR = \mathcal{E}/2R \times R = \mathcal{E}/2$$

$$V_B = IR = \mathcal{E}/2R \times R = \mathcal{E}/2$$

$$V_C = IR = 0 \times R = 0$$

[Bulb 'C' is in parallel]

d) POWER:Switch is open:

$$P_A = V_A I_A = \mathcal{E}/3 \times \mathcal{E}/3R$$

$$= \mathcal{E}^2/9R$$

$$P_A = P_B = P_C \text{ [power is same]}$$

Switch is closed:

$$P_A = V_A I_A = \mathcal{E}/2 \times \mathcal{E}/2R$$

$$P_A = \mathcal{E}^2/4R$$

$$P_B = V_B I_B = \mathcal{E}^2/4R$$

$$P_C = V_C I_C = 0$$

\therefore Total power will increase.

7. An electronics hobbyist is building a radio which requires 150Ω in her circuit. But she has only 220Ω , 79Ω and 92Ω resistors available. How can she connect the available resistors to get the desired value of resistance?

Solution

PG.NO:


7

MR.THIVYARAJ V.,M.Sc.,M.Phill.,M.Ed

Resistance required $R = 150 \Omega$

$R_1 = 220 \Omega$, $R_2 = 79 \Omega$


$R_3 = 92 \Omega$

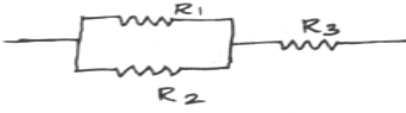

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{220 \times 79}{220 + 79}$$

$$R_p = \frac{17380}{299} = 58 \Omega$$

Now, R_p and R_3



$$R_s = R_p + R_3 = 58 + 92$$

$$\therefore R_s = 150 \Omega$$

Therefore , parallel combination of 230Ω and 79Ω in series with 92Ω

8. A cell supplies a current of 0.9 A through a 2Ω resistor and a current of 0.3 A through a 7Ω resistor. Calculate the internal resistance of the cell.

Solution

$$I_1 = 0.9 \text{ A} ; R_1 = 2 \Omega ; I_2 = 0.3 \text{ A} ; R_2 = 7 \Omega ; r = ?$$

$$I_1 = \frac{E}{R_1 + r} , E = I_1 [R_1 + r]$$

$$I_2 = \frac{E}{R_2 + r} ; E = I_2 [R_2 + r]$$

$$I_1 R_1 + I_1 r = I_2 R_2 + I_2 r$$

$$I_1 r - I_2 r = I_2 R_2 - I_1 R_1$$

$$r [I_1 - I_2] = I_2 R_2 - I_1 R_1$$

$$r = \frac{I_2 R_2 - I_1 R_1}{I_1 - I_2}$$

$$= \frac{0.3 \times 7 - 0.9 \times 2}{0.9 - 0.3}$$

$$= \frac{2.1 - 1.8}{0.6} = \frac{0.3}{0.6} = \frac{1}{2}$$



$$r = 0.5 \Omega$$

PG.NO:

8

MR.THIVIYARAJ V.,M.Sc.,M.Phil.,M.Ed

9. Calculate the currents in the following circuit.

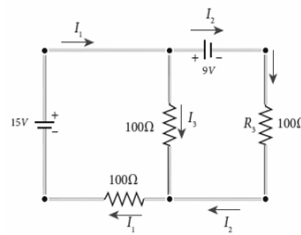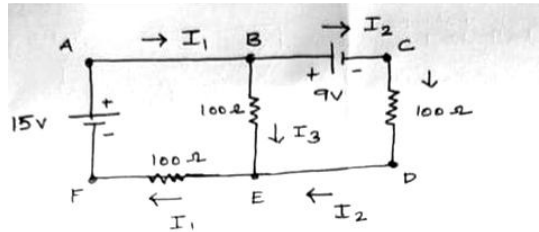Solution

$$I_1 = ? \quad ; \quad I_2 = ? \quad ; \quad I_3 = ?$$

Applying Kirchhoff's current rule at junction B.

$$I_1 - I_2 - I_3 = 0 \quad ; \quad I_3 = I_1 - I_2 \quad \text{--- (1)}$$

Applying Kirchhoff's Voltage rule for closed path ABEFA, $100I_1 + 100I_3 = 15$

$$100I_1 + 100[I_1 - I_2] = 15$$

$$100I_1 + 100I_1 - 100I_2 = 15$$

$$200I_1 - 100I_2 = 15 \quad \text{--- (2)}$$

Applying Kirchhoff's Voltage rule for closed path BCDEB,

$$100I_2 - 100I_3 = -9$$

$$100I_2 - 100[I_1 - I_2] = -9$$

$$100I_2 - 100I_1 + 100I_2 = -9$$

$$200I_2 - 100I_1 = -9$$

$$-100I_1 + 200I_2 = -9 \quad \text{--- (3)}$$

$$\text{(2)} \Rightarrow 200I_1 - 100I_2 = 15$$

$$\text{(3)} \times 2 \Rightarrow -200I_1 + 400I_2 = -18$$

$$\frac{300I_2 = -3}{100}$$

$$I_2 = \frac{-1}{10^2} = -1 \times 10^{-2} \Rightarrow I_2 = -0.01 \text{ A}$$

$$\text{(2)} \Rightarrow 200I_1 - 100 \times \frac{-1}{100} = 15$$

$$200I_1 + 1 = 15$$

$$200I_1 = 14 \quad ; \quad I_1 = \frac{14}{200}$$

$$I_1 = 0.07 \text{ A}$$

$$\text{(1)} \Rightarrow I_3 = I_1 - I_2$$

$$= 0.07 - [-0.01]$$

$$I_3 = 0.08 \text{ A}$$

PG.NO:

9

MR.THIVYARAJ V.,M.Sc.,M.Phill.,M.Ed

10. A potentiometer wire has a length of 4 m and resistance of $20\ \Omega$. It is connected in series with resistance of $2980\ \Omega$ and a cell of emf 4 V. Calculate the potential gradient along the wire.

GIVEN:

$$l = 4\text{ m}, \quad R = 20\ \Omega$$

$$\mathcal{E} = 4\text{ V}, \quad R' = 2980\ \Omega$$

$$E = ?$$

SOLUTION:

Effective resistance for two resistances in series combination. $R_s = R + R'$

$$R_s = 20 + 2980$$

$$R_s = 3000\ \Omega$$

$$I = \mathcal{E}/R = 4/3000\text{ A.}$$

∴ Potential drop across the wire,


$$V = IR; \quad V = I R = \frac{4}{3000} \times 20 = \frac{4}{150}\text{ Volt}$$

∴ Potential gradient, $E = V/l$

$$= \frac{4}{150} \times \frac{1}{4} = \frac{1}{150} = \frac{1}{15 \times 10} = 0.066 \times 10^{-1}$$

$$E = 0.66 \times 10^{-2}\text{ V m}^{-1}$$

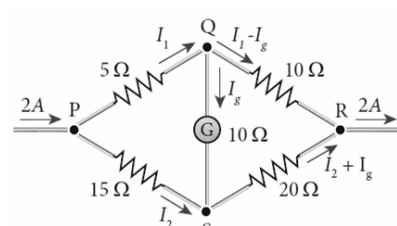
11. Determine the current flowing through the galvanometer (G) as shown in the figure.



PG.NO:

10

MR.THIVIYARAJ V.,M.Sc.,M.Phill.,M.Ed

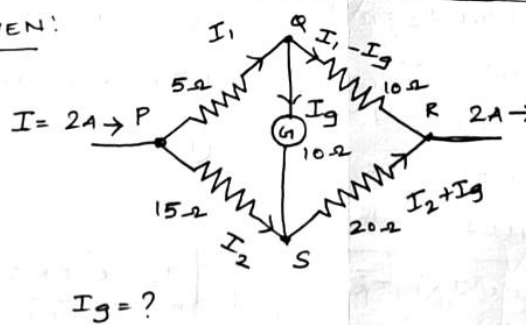SolutionGIVEN: $I_g = ?$ SOLUTION:

Applying Kirchhoff's Current rule at junction 'P'.

$$I - I_1 - I_2 = 0$$

$$I - I_1 = I_2 \rightarrow (1)$$

Apply Kirchhoff's Voltage rule for closed path PQSP.

$$5I_1 + 10I_g - 15I_2 = 0.$$

$$(1) \Rightarrow 5I_1 + 10I_g - 15[I - I_1] = 0.$$

$$5I_1 + 10I_g - 15I + 15I_1 = 0$$

$$I = 2A, \quad 20I_1 + 10I_g - 15 \times 2 = 0$$

$$20I_1 + 10I_g = 30 \rightarrow (2)$$

Apply Kirchhoff's Voltage rule for closed path QRSQ.

$$10[I_1 - I_g] - 20[I_2 + I_g] - 10I_g = 0.$$

$$10I_1 - 10I_g - 20I_2 - 20I_g - 10I_g = 0.$$

$$(1) \Rightarrow 10I_1 - 40I_g - 20[I - I_1] = 0.$$

$$10I_1 - 40I_g - 20I + 20I_1 = 0.$$

$$I = 2A, \quad 30I_1 - 40I_g - 20[2] = 0.$$

$$30I_1 - 40I_g = 40 \rightarrow (3)$$

$$(2) \times 3 \Rightarrow 60I_1 + 30I_g = 90.$$

$$(3) \times 2 \Rightarrow \begin{array}{r} 60I_1 \\ [-] \end{array} - 80I_g = 80 \quad \begin{array}{r} [+ \\ -] \end{array}$$


$$110I_g = 10$$

$$I_g = \frac{10}{110} = \frac{1}{11}$$

$$I_g = \frac{1}{11} A$$

12. Two cells each of 5V are connected in series with a $8\ \Omega$ resistor and three parallel resistors of $4\ \Omega$, $6\ \Omega$ and $12\ \Omega$. Draw a circuit diagram for the above arrangement. Calculate i) the current drawn from the cells (ii) current through each resistor

Solution

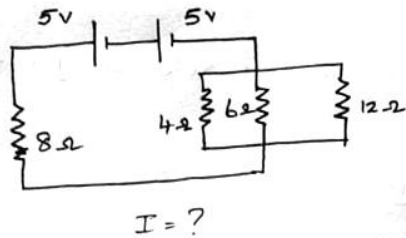


SOLUTION:

$$R_1 = 4\ \Omega ; R_2 = 6\ \Omega ; R_3 = 12\ \Omega$$

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} = \frac{3+2+1}{12}$$

$$\frac{1}{R_P} = \frac{6}{12} \Rightarrow R_P = 2\ \Omega$$

$$R_P = 2\ \Omega$$

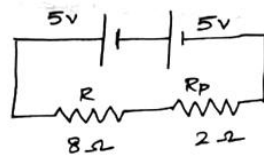

$$R_S = R + R_P$$

$$R_S = 8 + 2 = 10\ \Omega$$

$$R_S = 10\ \Omega$$

$$\mathcal{E} = \mathcal{E}_1 + \mathcal{E}_2 = 5 + 5 = 10\text{V.}$$

\therefore current drawn from each cell,

$$I = \mathcal{E} / R_S = 10 / 10 = 1\text{A.}$$

Potential ^{diff.} through $8\ \Omega$ resistor is $V = IR$

$$V = 1 \times 8 = 8\text{V}$$

\therefore Potential through $2\ \Omega$; $V = IR = 1 \times 2 = 2\text{V}$

(i) CURRENT through $8\ \Omega$; $I = \frac{V}{R} = \frac{8}{8}$; $I = 1\text{A}$

(ii) CURRENT through $4\ \Omega, 6\ \Omega, 12\ \Omega$;

$$R = 4\ \Omega ; I = \frac{V}{R} = \frac{2}{4} ; R = 6\ \Omega ; I = \frac{V}{R} = \frac{2}{6} ; R = 12\ \Omega ; I = \frac{V}{R} = \frac{2}{12}$$

$$I = 0.5\text{A}$$

$$I = 0.33\text{A}$$

$$I = 0.166\text{A}$$

PG.NO:

12

MR.THIVYARAJ V.,M.Sc.,M.Phill.,M.Ed


13. Four bulbs P, Q, R, S are connected in a circuit of unknown arrangement.

When each bulb is removed one at a time and replaced, the following behaviour is observed.

	P	Q	R	S
P removed	*	on	on	on
Q removed	on	*	on	off
R removed	off	off	*	off
S removed	on	off	on	*

Draw the circuit diagram for these bulbs.

Solution

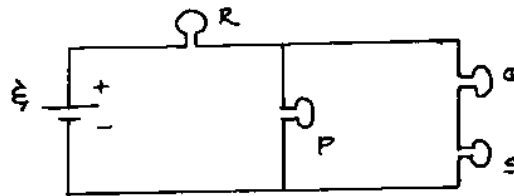

14. In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63 cm, what is the emf of the second cell?

Solution

GIVEN: $\mathcal{E}_1 = 1.25 \text{ V}$; $\mathcal{E}_2 = ?$ $\mathcal{E}_1 = 5/4 \text{ V}$.

$r_1 = 35 \times 10^{-2} \text{ m}$; $r_2 = 63 \times 10^{-2} \text{ m}$.

SOLUTION:

$$\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{r_2}{r_1} ; \mathcal{E}_2 = \mathcal{E}_1 \times \frac{r_2}{r_1}$$

$$\mathcal{E}_2 = \frac{5}{4} \times \frac{63 \times 10^{-2}}{35 \times 10^{-2}} = \frac{9}{4} = 2.25$$

$\mathcal{E}_2 = 2.25 \text{ Volt}$



www.Padasalai.Net

படங்களை தொடுக! பாடசாலை வலைதளத்தை சமூக ஊடகங்களில் பின்தொடர்க!! உடனுக்குடன் புதிய செய்திகளை Notifications-ல் பெறுக!



YouTube



Zoom



Touch Below Links



Download!

12th Standard	Syllabus	Books	Study Materials – EM	Study Materials - TM	Practical	Online Test (EM & TM)
	Monthly Q&A	Mid Term Q&A	Revision Q&A	PTA Book Q&A	Centum Questions	Creative Questions
	Quarterly Exam	Half Yearly Exam	Public Exam	NEET		

11th Standard	Syllabus	Books	Study Materials – EM	Study Materials - TM	Practical	Online Test (EM & TM)
	Monthly Q&A	Mid Term Q&A	Revision Q&A	Centum Questions	Creative Questions	
	Quarterly Exam	Half Yearly Exam	Public Exam	NEET		

10th Standard	Syllabus	Books	Study Materials - EM	Study Materials - TM	Practical	Online Test (EM & TM)
	Monthly Q&A	Mid Term Q&A	Revision Q&A	PTA Book Q&A	Centum Questions	Creative Questions
	Quarterly Exam	Half Yearly Exam	Public Exam	NTSE	SLAS	

9th Standard	Syllabus	Books	Study Materials	1st Mid Term	2nd Mid Term	3rd Mid Term
	Quarterly Exam	Half Yearly Exam	Annual Exam	RTE		

8th Standard	Syllabus	Books	Study Materials	1st Mid Term	2nd Mid Term	3rd Mid Term
	Term 1	Term 2	Term 3	Public Model Q&A	NMMS	Periodical Test

7th Standard	Syllabus	Books	Study Materials	1st Mid Term	2nd Mid Term	3rd Mid Term
	Term 1	Term 2	Term 3	Periodical Test	SLAS	

6th Standard	Syllabus	Books	Study Materials	1st Mid Term	2nd Mid Term	3rd Mid Term
	Term 1	Term 2	Term 3	Periodical Test	SLAS	

1st to 5th Standard	Syllabus	Books	Study Materials	Periodical Test	SLAS	
	Term 1	Term 2	Term 3	Public Model Q&A		

Exams	TET	TNPSC	PGTRB	Polytechnic	Police	Computer Instructor
	DEO	BEO	LAB Asst	NMMS	RTE	NTSE

Portal	Matrimony	Mutual Transfer	Job Portal
---------------	---------------------------	---------------------------------	----------------------------

Volunteers	Centum Team	Creative Team	Key Answer Team
-------------------	-----------------------------	-------------------------------	---------------------------------

Downloads	LESSON PLAN	Department Exam	Income Tax	Forms & Proposals	Fonts	Downloads
	Proceedings	GO's	Regulation Orders	Pay Orders	Panel	



Padasalai – Official Android App – [Download Here](#)



Kindly Send Your Study Materials, Q&A to our Email ID – Padasalai.net@gmail.com