


1R

UNIT - 2 CURRENT ELECTRICITY

ONE MARK QUESTIONS SOLUTION (BOOK BACK)

(For Questions Refer the book)

1) (a)

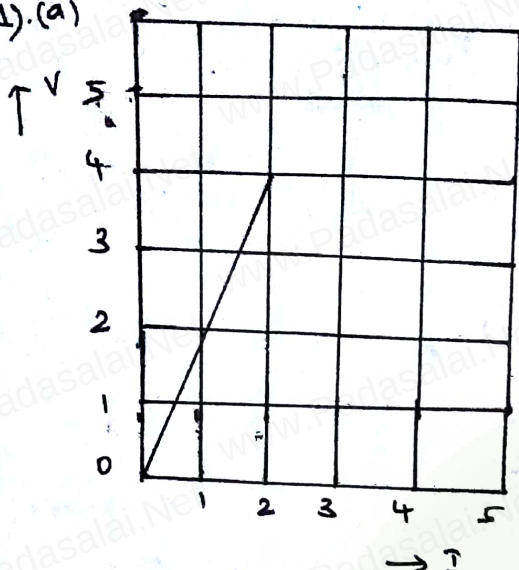

$$\text{Slope} = \frac{\Delta V}{\Delta I} = R = \frac{4-0}{2-0} = \frac{4}{2} = 2 \text{ ohm}$$

Ans: 2 ohm

resistance b/w two points A and B (Parallel combination)

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{2\pi \times 2\pi}{2\pi + 2\pi}$$

$$= \frac{4\pi^2}{4\pi}$$

$$R_p = \pi \text{ ohm.}$$

3) (c)

$$V = 240 \text{ V} ; R = 120 \Omega$$

$$P = ?$$

$$P = \frac{V^2}{R} = \frac{240 \times 240}{120}$$

$$P = 480 \text{ W}$$

2) a)

$$a = 1 \text{ m} ; R/a = 2 \text{ ohms}$$



$$\text{Circumference of the coil} = 2\pi a = 2\pi \times 1$$

$$= 2\pi \text{ metre}$$

$$\text{Resistance per unit length} = 2 \text{ ohms}$$

$$\text{Resistance through the circumference of the wire (R)} = 2 \times 2\pi$$

$$= 4\pi \text{ metre}$$

$$\text{Resistance at each section} = R' = R/2$$

(for semicircle)

$$R' = \frac{4\pi}{2} = 2\pi \text{ ohms.}$$

4) b)

$$(47 \pm 4.7) \text{ k}\Omega \quad (k = 10^3)$$

$$= (47000 \pm 4.7 \times 10^3) \Omega$$

$$= (47000 \pm 4700) \Omega$$

$$= (47000 \pm 10\%) \Omega$$

$$\text{color: } = (47 \times 10^3 \pm 10\%) \Omega$$

$$4 \Rightarrow \text{Yellow}$$

$$7 \Rightarrow \text{Violet}$$

$$10^3 \Rightarrow 3 \rightarrow \text{orange}$$

$$10\% \Rightarrow \text{silver}$$

$$\Rightarrow \text{Yellow - Violet - Orange - Silver.}$$

5) a)

$$\text{Brown} \Rightarrow 1$$

$$\text{Black} \Rightarrow 0$$

$$\text{Yellow} \Rightarrow 4 \Rightarrow 10^4$$

$$\text{value} = 10 \times 10^4$$

$$R = 100 \text{ k}\Omega$$

b) c)

$$l_1 = l_2 = l$$

Same material $P_1 = P_2 = P$

$$R_A = 3R_B ; r_A / r_B = ?$$

Same material

$$P_1 = P_2$$

$$\frac{R_A A}{l} = \frac{R_B A}{l}$$

$$R_A \pi r_A^2 = R_B \pi r_B^2$$

$$\frac{r_A^2}{r_B^2} = \frac{R_B}{R_A} = \frac{R_B}{3R_B}$$

$$\frac{r_A^2}{r_B^2} = \frac{1}{3}$$

$$\boxed{\frac{r_A}{r_B} = \left(\frac{1}{3}\right)^{1/2} = \frac{1}{\sqrt{3}}}$$

Power dissipation

$$P_2 = \frac{V^2}{R_P} = \frac{V^2}{R/4}$$

$$P_2 = \frac{4V^2}{R}$$

ratio

$$\frac{P_2}{P_1} = \frac{4V^2}{R} \times \frac{R}{V^2}$$

$$\boxed{P_2/P_1 = 4}$$

8) (c)

In India and USA the power of the bulb is using a same

(given)

$$V_1 = 220V \text{ (India)}$$

$$P_1 = 60W$$

$$R_1 = R$$

$$V_2 = 110V \text{ (USA)}$$

$$P_2 = 60W$$

$$R_2 = ?$$

$$P_1 = P_2$$

$$\frac{V_1^2}{R_1} = \frac{V_2^2}{R_2}$$

$$R_2 = \frac{V_2^2}{V_1^2} \times R_1$$

$$= \frac{110 \times 110}{220 \times 220} \times R$$

$$\boxed{R_2 = \frac{R}{4}}$$

7) d)

$$V = 230V$$

$$\text{Power dissipation } P_1 = \frac{V^2}{R_1} = \frac{V^2}{R}$$

If the wire cut into two equal pieces then resistance will be halved.

$$\text{So, the resistance of wire 1} = R/2$$

$$\text{" wire 2} = R/2$$

Then two wire is connected parallel with same power supply (230V)

$$R_P = \frac{R_1 R_2}{R_1 + R_2} = \frac{R/2 \times R/2}{R/2 + R/2}$$

$$= \frac{R^2/4}{2R/2}$$

$$\boxed{R_P = R/4 \text{ ohm}}$$

9) d)

$$\text{Total Power } P = (n_1 P_1) + (n_2 P_2) + (n_3 P_3) + (n_4 P_4)$$

$$= (15 \times 40) + (5 \times 100) + (5 \times 80) + (1 \times 1000)$$

$$= 600 + 500 + 400 + 1000$$

$$P = 2500W$$

$$V = 220V$$

$$P = VI$$

$$I = P/V = \frac{2500}{220}$$

$$I = 11.3$$


$$I \approx 12A$$

$$V = IR_p$$

$$I = V/R_p = \frac{5}{5}$$

$$I = 1A$$

10) c)

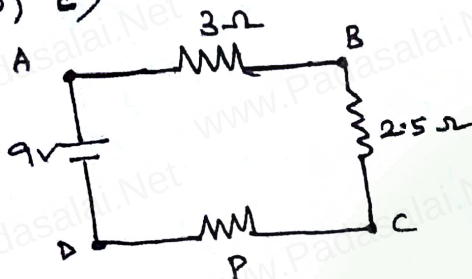

Applying Kirchhoff's 2nd law for a closed loop ABCDA

$$3I + 2.5I + PI = 9$$

$$5.5I + PI = 9$$

$$(5.5 + P)I = 9 \quad [I = 1A]$$

$$5.5 + P = 9$$

$$P = 9 - 5.5$$

$$P = 3.5\Omega$$

12) d)

$$\alpha = 0.00125/^{\circ}C$$

$$t_1 = 300K = 27^{\circ}C$$

$$t_2 = ?$$

$$R_{t1} = 1\Omega; R_{t2} = 2\Omega$$

$$R_{t1} = R_0(1 + \alpha t_1)$$

$$R_{t2} = R_0(1 + \alpha t_2)$$

$$\frac{R_{t2}}{R_{t1}} = \frac{2}{1} = \frac{1 + \alpha t_2}{1 + \alpha t_1}$$

$$2(1 + \alpha t_1) = 1 + \alpha t_2$$

$$2 + 2\alpha t_1 = 1 + \alpha t_2$$

$$\alpha t_2 - 2\alpha t_1 = 1$$

$$\alpha(t_2 - 2t_1) = 1$$

$$t_2 - 2t_1 = \frac{1}{\alpha}$$

$$t_2 = \frac{1}{\alpha} + 2t_1$$

$$= \frac{1}{0.00125} + 2(27)$$

$$= \frac{10^5}{125} + 54$$


$$= 800 + 54$$

$$t_2 = 854^{\circ}C$$

$$t_2 = 854 + 273$$

$$t_2 = 1127K$$

11) a)

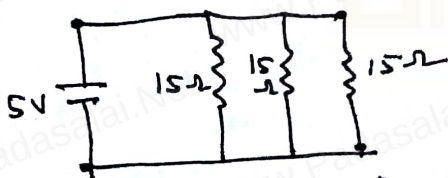

Resistors are connected with Power Supply in Parallel combination

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{15} + \frac{1}{15} + \frac{1}{15}$$

$$\frac{1}{R_p} = \frac{3}{15}$$

$$R_p = 15/3 = 5\Omega$$

13) b)

$$\Sigma_f = 2.1V; I = 0.2A; R = 10\Omega$$

$$V = IR = 0.2 \times 10 = 2V$$

$$r = \left(\frac{\Sigma_f - V}{V} \right) R = \left(\frac{2.1 - 2}{2} \right) 10 = 0.5\Omega$$

14) d)

* Copper has positive temperature coefficient of resistance

So, resistance decreases with decrease in temperature.

* Germanium has negative temperature co-efficient of resistance.

So, resistance increases with decrease in temperature.

For room temperature to 80 K
The resistance of Copper
decreases and of germanium
increases.

15)

For given current (I) and time (t) the heat is directly proportional to square of current

$$H \propto I^2$$

So the graph will be straight line.