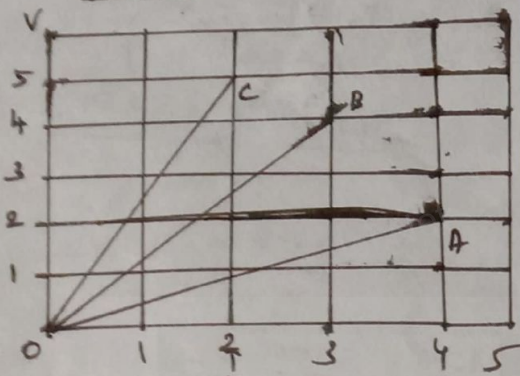


XII

UNIT-2 [Current Electricity]

Exercise Problems

1 Figure 1: (Graph 1)



According to Ohm's law

$$V = IR$$

$$R = V/I$$

For A

$$R_A = \frac{\Delta V}{\Delta I} = \frac{2-0}{4-0} = \frac{2}{4} = 0.5 \Omega$$


For B

$$R_B = \frac{\Delta V}{\Delta I} = \frac{4-0}{3-0} = \frac{4}{3} = 1.33 \Omega$$

For C

$$R_C = \frac{\Delta V}{\Delta I} = \frac{5-0}{2-0} = \frac{5}{2} = 2.5 \Omega$$

Graph 2:

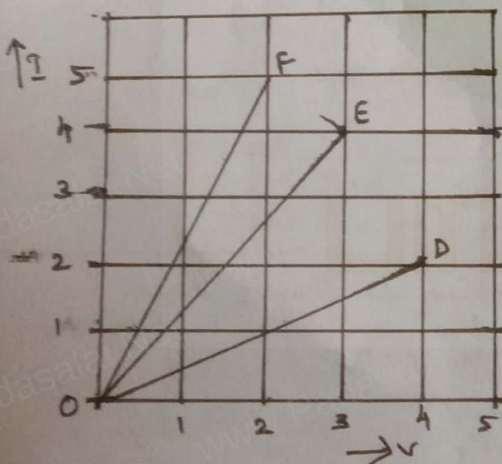

In graph 2

$$\text{Slope} = \frac{\Delta I}{\Delta V}$$

$$R = \frac{1}{\text{slope}} = \frac{\Delta V}{\Delta I}$$

For D

$$R_D = \frac{\Delta V}{\Delta I} = \frac{4-0}{2-0} = \frac{4}{2} = 2 \Omega$$

For E:

$$R_E = \frac{\Delta V}{\Delta I} = \frac{3-0}{4-0} = \frac{3}{4} = 0.75 \Omega$$

For F:

$$R_F = \frac{\Delta V}{\Delta I} = \frac{2-0}{5-0} = \frac{2}{5} = 0.4 \Omega$$

From A, B, C, D, E and F

R_F has minimum resistance
 R_C has maximum resistance

2 $W = 10^9 \text{ J}$; $V = 5 \times 10^7 \text{ V}$

$$t = 0.2 \text{ s}$$

a) Total amount of charge transferred

$$W = Vq$$

$$q = \frac{W}{V} = \frac{10^9}{5 \times 10^7} = 0.2 \times 10^2$$

$$q = 20 \text{ C}$$

b) the current in the lightning bolt

$$I = \frac{q}{t} = \frac{20}{0.2} = \frac{20}{2 \times 10^{-1}}$$

$$I = 100 \text{ A}$$

c) the power delivered in 0.2 s

$$P = VI = 5 \times 10^7 \times 100 = 5 \times 10^9$$

$$P = 5 \text{ GW}$$

3 $A = 10^{-6} \text{ m}^2$; $I = 2 \text{ A}$

$$n = 8 \times 10^{28}$$

$$J = ? \quad V_d = ?$$

$$J = \frac{I}{A}$$

$$= \frac{2}{10^{-6}}$$

$$J = 2 \times 10^6 \text{ Am}^{-2}$$

$$J = nev_d$$

$$v_d = \frac{J}{ne} = \frac{2 \times 10^6}{8 \times 10^{28} \times 1.6 \times 10^{-19}}$$

$$= 0.156 \times 10^{-3}$$

$$v_d = 15.6 \times 10^{-5} \text{ ms}^{-1}$$

④ $R_0 = 10 \Omega$; $\alpha = 0.004/^{\circ}\text{C}$
 $R_{100} = ?$ $T = 100^{\circ}\text{C}$; $T_0 = 0^{\circ}\text{C}$

$$R_T = R_0 (1 + \alpha (T - T_0))$$


$$R_{100} = 10 (1 + 0.004 (100))$$

$$= 10 (1 + 0.4)$$

$$= 10 (1.4)$$

$$R_{100} = 14 \Omega$$

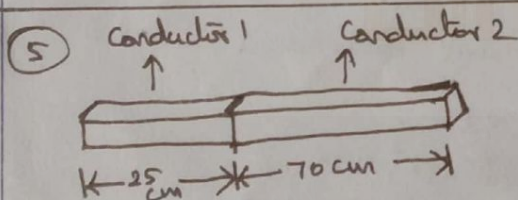As the temperature increases the resistance of the wire also increases



$$P_1 = 4 \times 10^{-3} \Omega \text{ m}; l_1 = 25 \times 10^{-2} \text{ m}$$

Area = multiplication of length of 2 sides

$$= 3 \times 10^{-3} \times 3 \times 10^{-3}$$

$$A = 9 \times 10^{-6} \text{ m}^2$$

$$P_2 = 5 \times 10^{-3} \Omega \text{ m}; l_2 = 70 \times 10^{-2} \text{ m}$$

$$R = ? \text{ (between the rods)}$$

$$R_s = R_1 + R_2$$

$$R_1 = \frac{P_1 l_1}{A}$$

$$= \frac{4 \times 10^{-3} \times 25 \times 10^{-2}}{9 \times 10^{-6}}$$

$$= \frac{100 \times 10^{-5}}{9 \times 10^{-6}}$$

$$R_1 = \frac{1000}{9} \Omega$$

$$R_2 = \frac{P_2 l_2}{A}$$

$$= \frac{5 \times 10^{-3} \times 70 \times 10^{-2}}{9 \times 10^{-6}}$$

$$= \frac{350 \times 10^{-5} \times 10^6}{9}$$

$$R_2 = \frac{3500}{9} \Omega$$

$$R_s = R_1 + R_2$$

$$= \frac{1000}{9} + \frac{3500}{9}$$

$$= \frac{4500}{9}$$

$$R_s = 500 \Omega$$

⑥ According to Ohm's law

a) $V = IR$

$$V = \sum V$$

$$R_1 = R_2 = R_3 = R$$

Three bulbs are connected in series combination

$$R_s = R_1 + R_2 + R_3$$

$$R_s = R + R + R = 3R$$

When Switch open:

$$I = \frac{V}{R_s} = \frac{\sum \epsilon}{3R}$$

When Switch closed:

$$I = \frac{V}{RR} = \frac{\sum \epsilon}{R+R}$$

$$I = \frac{\sum \epsilon}{2R}$$

When "s" closed no current flows through c bulb.

b) When Switch open

Three bulbs are in series combination so there is no change in intensities.

So all the bulbs having equal intensities.

When Switch closed:

Two bulbs A and B are only in series combination so the intensities across two bulbs (A and B) increases and both having equal intensities.

The bulb "c" is in parallel combination, hence no current flows through c bulb, so it will not glow.

c) voltage:

Switch is open:

In series combination the current will same.

So

$$V_A = IR = \frac{\sum \epsilon}{3R} \cdot R$$

$$V_A = \frac{\sum \epsilon}{3}$$

$$V_B = IR = \frac{\sum \epsilon}{3R} \cdot R$$

$$V_B = \frac{\sum \epsilon}{3}$$

$$V_c = IR = \frac{\sum \epsilon}{3R} \cdot R$$

$$V_c = \frac{\sum \epsilon}{3}$$

Switch closed:

both A and B are in series combination. bulb c in parallel so no current flows through c so $I=0$

$$V_A = IR = \frac{\sum \epsilon}{2R} \cdot R$$

$$V_A = \frac{\sum \epsilon}{2}$$

$$V_B = IR = \frac{\sum \epsilon}{2R} \cdot R$$

$$V_B = \frac{\sum \epsilon}{2}$$

$$V_c = IR = 0 \times R$$

$$V_c = 0$$

d) Power: Switch open:

$$V_A = IR \quad P_A = V_A I_A = \frac{\sum \epsilon}{3} \times \frac{\sum \epsilon}{3R}$$

$$P_A = \frac{\sum \epsilon^2}{9R}$$

$$P_B = V_B I_B = \frac{\sum \epsilon}{3} \times \frac{\sum \epsilon}{3R} = \frac{\sum \epsilon^2}{9R}$$

$$P_c = V_c I_c$$

$$= \frac{V_c}{3} \times \frac{V_c}{3R}$$

$$P_c = \frac{V_c^2}{9R}$$

Switch closed.

$$P_A = V_A I_A$$

$$= \frac{V_c}{2} \times \frac{V_c}{2R}$$

$$P_A = \frac{V_c^2}{4R^2}$$


$$P_B = V_B I_B$$

$$= \frac{V_c}{2} \times \frac{V_c}{2R}$$

$$P_B = \frac{V_c^2}{4R^2}$$

$$P_c = V_c I_c$$

$$P_c = 0$$

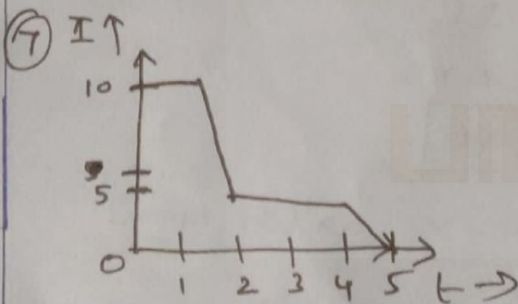

At $t=0s$

$$I = \frac{dq}{dt}$$

$$dq = I \times dt$$

$$dq = 0s$$

At $t=2s$

$$I = \frac{dq}{dt}$$

$$dq = I \times dt = 5 \times 2$$

$$dq = 10C$$

At $t=5s$

$$I = \frac{dq}{dt} \Rightarrow dq = I \times dt$$

$$dq = 0 \times 5 = 0s$$

8 resistance of required } = 150\Omega

$$R_1 = 220\Omega; R_2 = 79\Omega; R_3 = 92\Omega$$

For getting 150\Omega resistance as resultant, two of the resistance should be connected in parallel and 1 connected with series.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{220} + \frac{1}{79}$$

$$R_p = \frac{220 \times 79}{220 + 79} = \frac{17380}{299}$$

$$= 58.1$$

$$R_p \approx 58\Omega$$

$$R_s = R_p + R_3$$

$$= 58 + 92$$

$$R_s = 150\Omega$$

9 $I_1 = 0.9A; R_1 = 2\Omega$

$$I_2 = 0.3A; R_2 = 7\Omega$$

$$r = ?$$

$$I_1 = \frac{V}{R_1 + r}$$

$$V = I_1 (R_1 + r) \quad (1)$$

$$V = I_2 (R_2 + r) \quad (2)$$

$$I_1 (R_1 + r) = I_2 (R_2 + r)$$

$$I_1 R_1 + I_1 r = I_2 R_2 + I_2 r$$


$$I_1 R_1 - I_2 R_2 = I_2 r - I_1 r$$

$$r = \frac{I_1 R_1 - I_2 R_2}{I_2 - I_1}$$

$$r = \frac{(0.9 \times 2) - (0.3 \times 7)}{0.3 - 0.9}$$

$$r = \frac{1.8 - 2.1}{-0.6} = \frac{-0.3}{-0.6} = \frac{0.3}{0.6} = 0.5\Omega$$

10

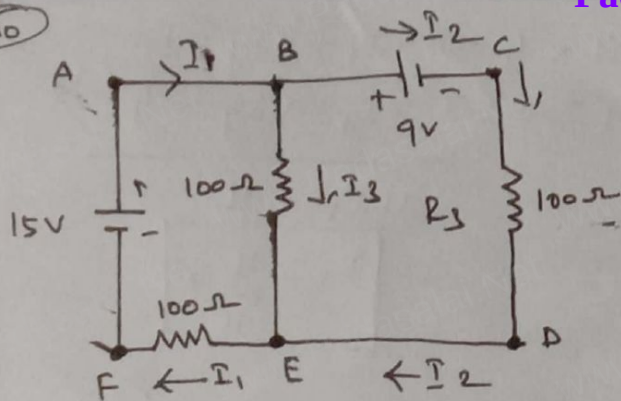

Kirchoff's law (1st law) at junction B

$$I_1 - I_2 - I_3 = 0$$

$$I_3 = I_1 - I_2 \quad (1)$$

Kirchoff's II law in ABEFA

$$100I_3 + 100I_1 = 15V$$

$$100(I_1 - I_2) + 100I_1 = 15V$$

$$100I_1 - 100I_2 + 100I_1 = 15$$

$$200I_1 - 100I_2 = 15 \quad (2)$$

Kirchoff's II law in BCDEB

$$100I_3 - 100I_2 = 9$$

$$100(I_1 - I_2) - 100I_2 = 9$$

$$100I_1 - 100I_2 - 100I_2 = 9$$

$$100I_1 - 200I_2 = 9 \quad (3)$$

$$(2) \times 2 \Rightarrow 200I_1 - 400I_2 = 18$$

$$(3) \Rightarrow 200I_1 - 100I_2 = 15$$

$$-300I_2 = +3$$

$$I_2 = -\frac{3}{300}$$

$$I_2 = -0.01A$$

Substitute I_2 in eqn. No. (2)

$$200I_1 - 100(-0.01) = 15$$

$$200I_1 + 1 = 15$$

$$200I_1 = 14$$

$$I_1 = \frac{14}{200} = \frac{7}{100}$$

$$I_1 = 0.07A$$

Substitute I_1 & I_2 in eqn. (1)

$$I_3 = 0.07 - (-0.01)$$

$$I_3 = 0.08A$$

$$(11) \quad r = 20\Omega ; \quad l = 4m.$$

$$\Sigma r = 4V ; \quad R' = 2980\Omega$$

Effective resistance of two resistors in series combination

$$R = r + r'$$

$$= 20 + 2980$$

$$R = 3000\Omega$$

$$I = \Sigma r / R = \frac{4}{3000} A$$

Potential drop across the wire

$$V = I \times r$$

$$= \frac{4}{3000} \times 20$$

$$V = \frac{80}{3000} V \Rightarrow V = \frac{8}{300} V$$

Potential gradient (E) = V/l .


$$= \frac{80}{3000} \times \frac{1}{4}$$

$$= \frac{2}{3000}$$

$$= 0.00066$$

$$E = 0.0066$$

$$E = 0.66 \times 10^{-2} Vm^{-1}$$

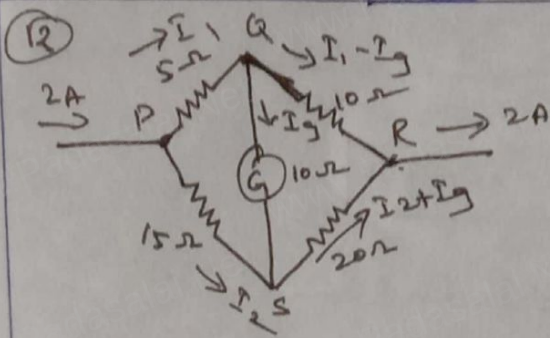

$$I = 2A$$

$$I_2 = I - I_1$$

Applying Kirchhoff's I law at P & S

$$5I_1 + 10I_g - 15I_2 = 0$$

$$5I_1 + 10I_g - 15(I - I_1) = 0$$

$$5I_1 + 10I_g - 15I + 15I_1 = 0$$

$$20I_1 - 15I + 10I_g = 0$$

$$20I_1 - 30 + 10I_g = 0$$

$$20I_1 + 10I_g = 30$$

$$2I_1 + I_g = 3 \quad \text{--- (1)}$$

Applying Kirchhoff's II law at QRSQ

$$10(I_1 - I_g) - 20(I_2 + I_g) - 10I_g = 0$$

$$10I_1 - 10I_g - 20I_2 - 20I_g - 10I_g = 0$$

$$10I_1 - 40I_g - 20I_2 = 0$$

$$10I_1 - 40I_g - 20(I - I_1) = 0$$

$$10I_1 - 40I_g - 20I + 20I_1 = 0$$

$$30I_1 - 40I_g - 20(2) = 0$$

$$30I_1 - 40I_g - 40 = 0$$

$$30I_1 - 40I_g = 40$$

$$3I_1 - 4I_g = 4 \quad \text{--- (2)}$$

$$(1) \times 4 \Rightarrow 8I_1 + 4I_g = 12 \quad (+)$$

$$(2) \Rightarrow 3I_1 - 4I_g = 4$$

$$11I_1 = 16$$

$$I_1 = \frac{16}{11} A$$

I_1 value substitute in (1)


$$2 \times \left(\frac{16}{11}\right) + I_g = 3$$

$$3.2 + 11I_g = 33$$

$$11I_g = 33 - 3.2$$

$$I_g = \frac{1}{11} A$$

13

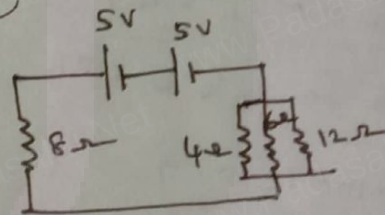

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12}$$

$$\frac{1}{R_p} = \frac{6+4+2}{24} = \frac{12}{24} = \frac{1}{2}$$

$$R_p = 2\Omega$$

$$R_s = R_p + R = 2 + 8$$

$$R_s = 10\Omega$$

$$\Sigma \mathcal{E} = \mathcal{E}_1 + \mathcal{E}_2$$

$$= 5 + 5$$

$$\Sigma \mathcal{E} = 10V$$

i) Current drawn from the cell

$$I = \frac{\Sigma}{R} = \frac{10}{10}$$

$$I = 1A$$

ii) Current through each resistor

Potential through 8Ω resistor

$$V = IR = 8 \times 1 = 8V$$

Potential through (parallel network)

2Ω resistor

$$V = IR = 1 \times 2$$

$$V = 2V$$

i) ~~Current~~ Current across 4Ω $I = \frac{V}{R} = \frac{2}{4}$

$$I = 0.5A$$


ii) across 6Ω $I = \frac{V}{R} = \frac{2}{6}$

$$I = 0.33A$$

iii) across 12Ω $I = \frac{V}{R} = \frac{2}{12}$

$$I = 0.17A$$

Ans:

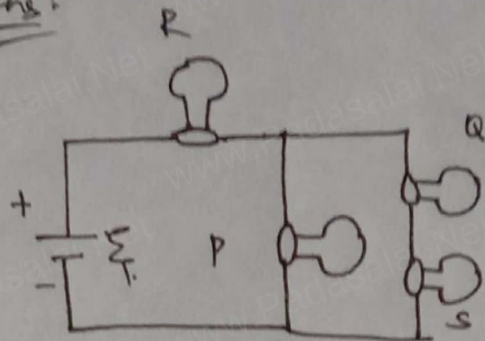

15) $\Sigma_1 = 1.25V$ $l_1 = 35cm$

$\Sigma_2 = ?$ $l_2 = 63cm$

$$\Sigma \propto l$$

$$\frac{\Sigma_1}{\Sigma_2} = \frac{l_1}{l_2}$$

$$\frac{\Sigma_2}{\Sigma_1} = \frac{l_2}{l_1}$$

$$\Sigma_2 = \Sigma_1 \frac{l_2}{l_1}$$

$$= 1.25 \times \frac{63 \times 10^{-2}}{35 \times 10^{-2}}$$

$$= 1.25 \times 10^{-2} \times \frac{63}{35}$$

$$= 1.25 \times 10^{-2} \times \frac{9}{5}$$

$$= 25 \times 9 \times 10^{-2}$$

$$= 225 \times 10^{-2}$$

$$\Sigma_2 = 2.25V$$

14

	P	Q	R	S
P removed	*	on	on	on
Q removed	on	*	on	off
R removed	off	off	*	off
S removed	on	off	on	*